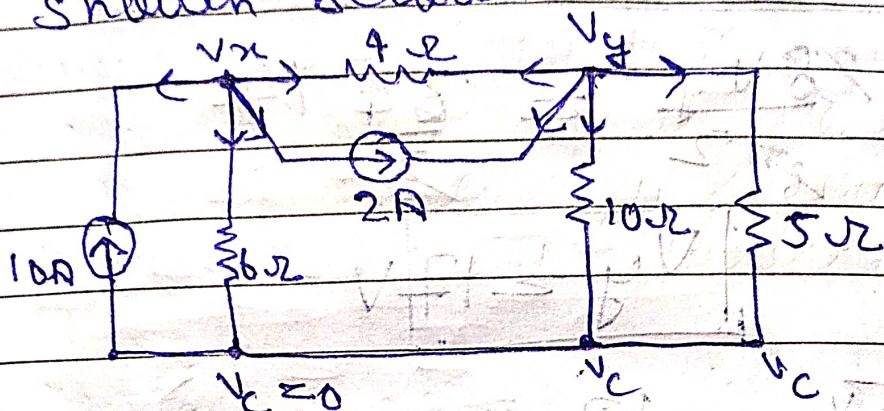


11 Dec 20

Tutorial Sheet - 1

- ① Find the node voltages (V_x) and (V_y) using nodal analysis for the circuit shown below



$$-10 + \frac{V_x}{6} + 2 + V_x - V_y = 0$$

$$\frac{V_x}{6} + \frac{V_x}{4} - \frac{V_y}{5} = 8$$

$$\frac{5V_x}{12} - \frac{V_y}{4} = 8 \quad \text{--- (1)}$$

$$\frac{V_y - V_c}{10} + \frac{V_y - V_c}{5} - 2 + \frac{V_y - V_x}{4} = 0$$

$$\frac{3V_y}{20} + \frac{V_y}{4} - \frac{V_x}{4} = 2$$

$$\frac{11V_y}{20} - \frac{V_x}{4} = 2 \quad \text{--- (1)}$$

$$\frac{11V_y}{5} - V_x = 8$$

Multiplying $\times \frac{5}{12}$ in Eq - (1)

Mayank Tandon
2012024
S-11

Date _____
Page _____

$$\frac{11V_y}{12} - \frac{5V_N}{12} = \frac{10}{12} = \frac{10}{3}$$

$$\frac{5V_N}{12} - V_y = \frac{8}{3}$$

$$\frac{28V_y}{36} = \frac{34}{3}$$

$$V_y = 17V$$

$$\frac{5V_N}{12} - \frac{17}{4} = 8$$

$$\frac{5}{12}V_N = 8 + 17$$

$$V_N = \frac{12}{5} \left[\frac{49}{4} \right]$$

$$V_N = \frac{147}{5} 29.04$$

$$V_N = 29.04V$$

$$\therefore V_y = 17V \text{ and } V_N = 29.04V$$


Mayank Johari

2012024

S-11

Date _____
Page _____

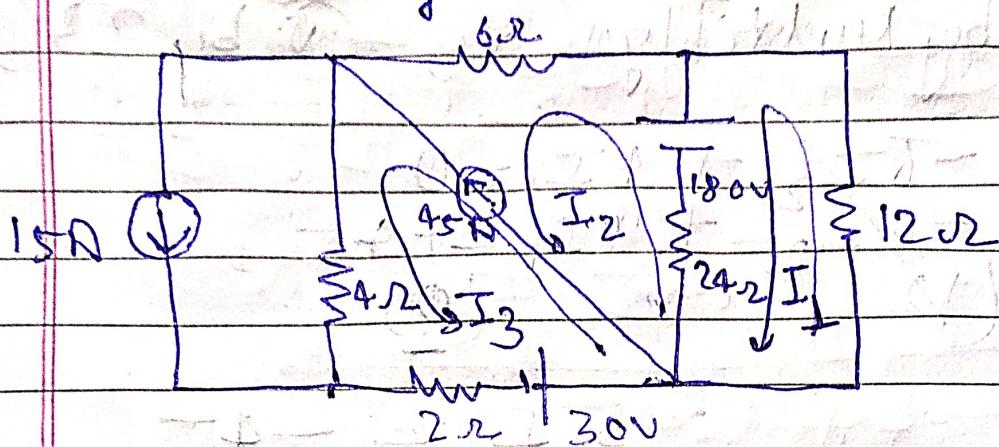- (2) Find the Current through 12Ω , using Mesh analysis for the Network.



Total 3 Mesh

Mesh-1

$$+12I_1 - 180 + 24(I_1 - I_2) = 0$$

$$12I_1 + 24I_1 - 24I_2 = 180$$

$$36I_1 - 24I_2 = 180$$

$$3I_1 - 2I_2 = 15 \quad (1)$$

Mesh-2

$$-24(I_2 - I_1) + 180 - 6I_2 - 4(I_3 - 15) - 2I_3 + 30 = 0$$

$$-24I_2 + 24I_1 + 180 - 6I_2 - 4I_3 + 60 - 2I_3 + 30 = 0$$

$$-30I_2 + 24I_1 - 6I_3 + 270 = 0 \quad (2)$$

$$I_3 - I_2 = 45 \quad (11)$$

$$I_3 = I_2 + 45$$

Putting the value of I_3 in Eq (11)

$$-30I_2 + 24I_1 + 270 - 6(I_2 + 45) = 0$$

$$-30I_2 + 24I_1 + 270 - 6I_2 - 270 = 0$$

Mayank Johari
2012.02.4

Date _____
Page _____

S-11

$$-3\beta I_2 + 24I_1 = 0 \quad (1)$$

$$-3I_2 + 2I_1 = 0 \quad (2)$$

by multiplying Eq - (2) by 2 & (1) by

$$-6I_2 + 4I_1 = 0$$

$$-6I_2 + 9I_1 = 45$$

$$(+) + (G) \quad (-) + (2)$$

$$-5I_1 = -45$$


$$I_1 = 9A$$

- Current through $R_{12,2}$ is 9A

- Current through $R_{12,2}$ is 9A


(2) Find the supply current using
Star-delta formation,

10V

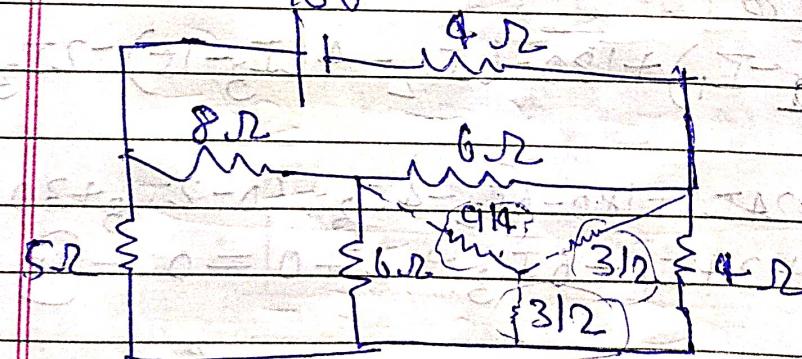

by using Delta to Star


10V

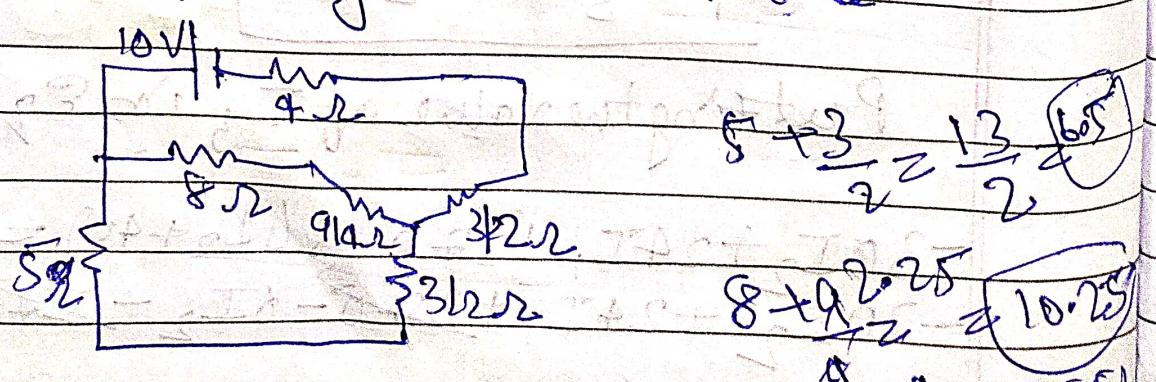


Mayank Sachdev
2012024

Date _____
Page _____

$$\frac{4+3}{2} \geq 5.5\sqrt{2}$$

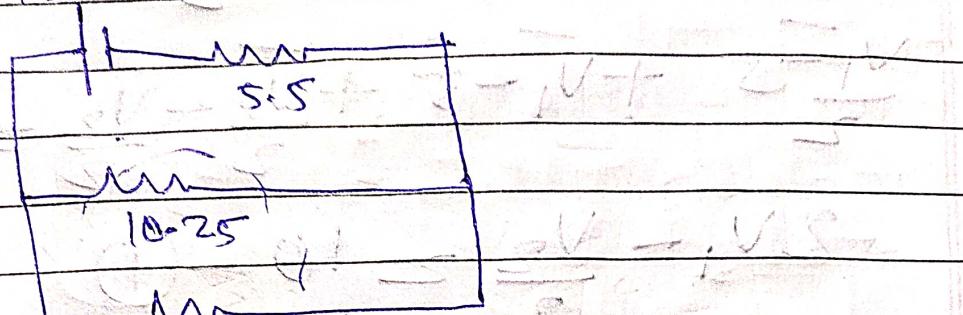
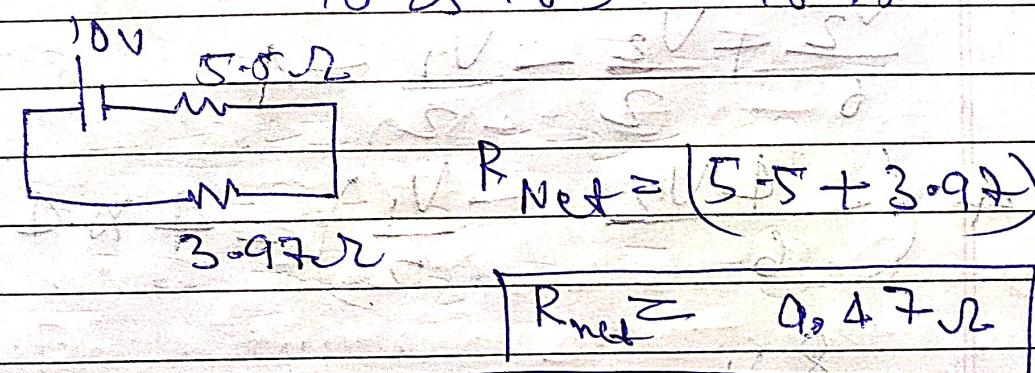
$$C = R \geq \frac{10.25 \times 6.5}{10.25 + 6.5} = \frac{66.625}{16.75} \geq 3.97\Omega$$




$$R_{\text{net}} = 9.47\Omega$$

$$I = \frac{V}{R_{\text{net}}} = \frac{10}{9.47} \approx 1.05 \text{ A}$$

$$I = 1.05 \text{ A}$$

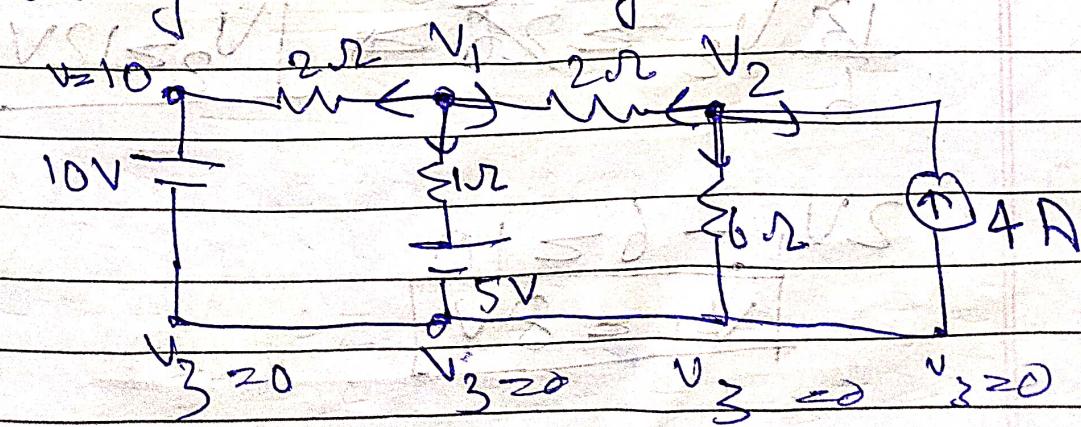- ④ Find the Node Voltages & branch currents using nodal analysis.



Mayank Johar
2012024

Date _____
Page _____

$$\frac{V_1 - 10}{2} + V_1 - 8 + \frac{V_1 - V_2}{2} \geq 0$$

$$\frac{V_1 - 8}{2} + V_1 - 8 + \frac{V_1 - V_2}{2} \geq 0$$

$$2V_1 - \frac{V_2}{2} \geq 10 \quad \text{(1)}$$

$$-4 + \frac{V_2 - V_1}{2} + \frac{V_2}{2} \geq 0$$

$$\frac{V_2}{6} + \frac{V_2}{2} - \frac{V_1}{2} \geq 4$$

$$4 \left(\frac{-4V_2}{6} + \frac{-V_1}{2} \right) \leq 4 \times 4$$

$$\frac{8V_2}{3} - 2V_1 \geq 16$$

$$\frac{-V_2}{2} + 2V_1 \geq 10$$

$$(16 - 3)V_2 \geq 26$$

$$\frac{13}{6}V_2 \geq 26 \Rightarrow V_2 \geq 12V$$

$$2V_1 - 6 \geq 10$$

$$V_1 = 8V$$

$$I_{2,2} = \frac{V_2 - V_1}{2} = \frac{12 - 4}{2} = 4 \text{ A}$$


$$I_{2,2} = 2 \text{ A}$$

$$I_{1,2} = \frac{V_1 - 5}{1} = 3 \text{ A}$$

$$I_{6,2} = \frac{12}{6} = 2 \text{ A}$$

$$I_{1,2} = \frac{10 - 8}{2} = 1 \text{ A}$$

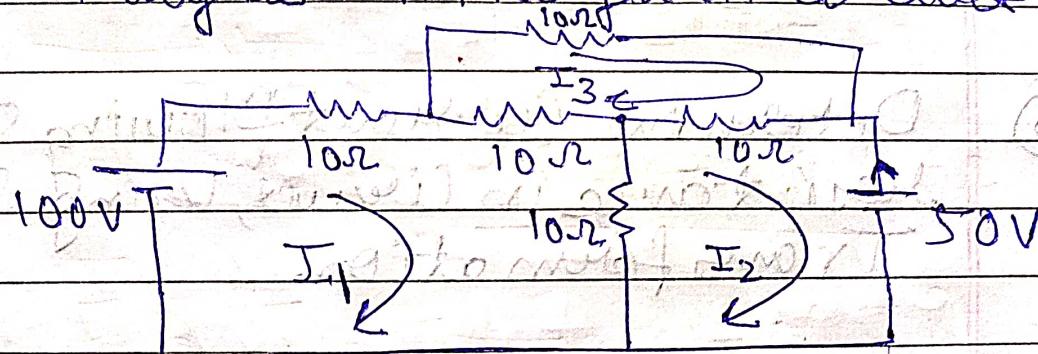- (5) Find the mesh Current using mesh analysis in the given circuit



Loop - I

$$100 - 10I_1 - 10(I_1 - I_3) - 10(I_1 - I_2) = 0$$

$$100 - 30I_1 + 10I_2 + 10I_3 = 0$$

$$10 - 3I_1 + I_2 + I_3 = 0 \quad \text{(1)}$$

Loop - II

$$-10(I_2 - I_3) - 50 - 10(I_2 - I_3) = 0$$

$$20I_2 + 10I_3 + 10I_1 = 50$$

$$I_1 + 2I_2 + I_3 - 50 = 0 \quad \text{(II)}$$

Loop - ③

$$\begin{aligned} -10I_3 - 10L(I_3 - I_2) - 10(I_3 - I_1) &= 0 \\ -10I_3 - 10I_2 + 10I_1 - 10I_3 + 10I_2 &= 0 \\ \therefore -30I_3 + 10I_1 + 10I_2 &\geq 0 \\ -3I_3 + I_2 + I_1 &\geq 0 \quad \text{(11)} \end{aligned}$$


by solving eq - ⑩, ⑪ & ⑫

$$I_1 = -3.75 \text{ A}$$


$$I_2 = 0 \text{ A}$$

$$I_3 = 1.25 \text{ A}$$

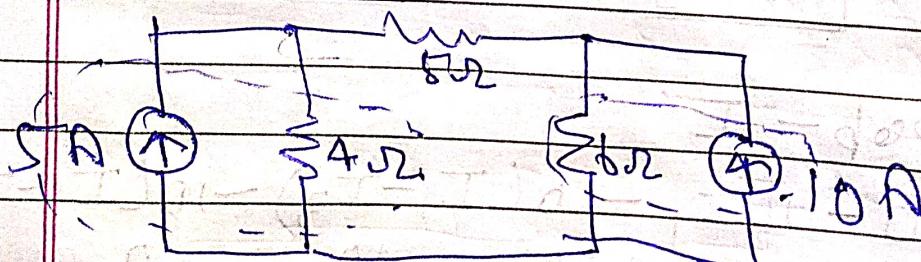- ⑥ Determine Current flowing in 5Ω resistance in Circuit, using Source Transformation.



by using Source Transformation

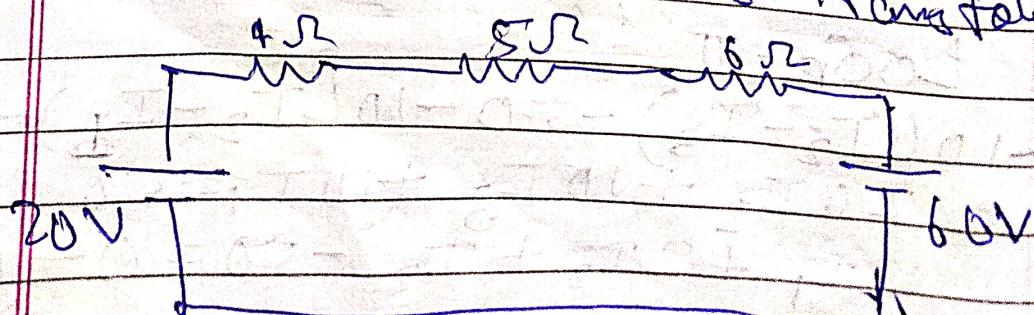


Mayank Johari 134

2012024

Date _____
Page _____

15Ω

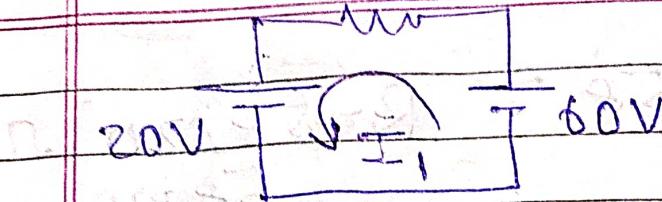


$$60 - 15I_1 - 20 = 0$$

$$40 = 15I_1$$


$$I_1 = \frac{40}{15} = 2.67A$$

∴ Current through SR is 2.67A

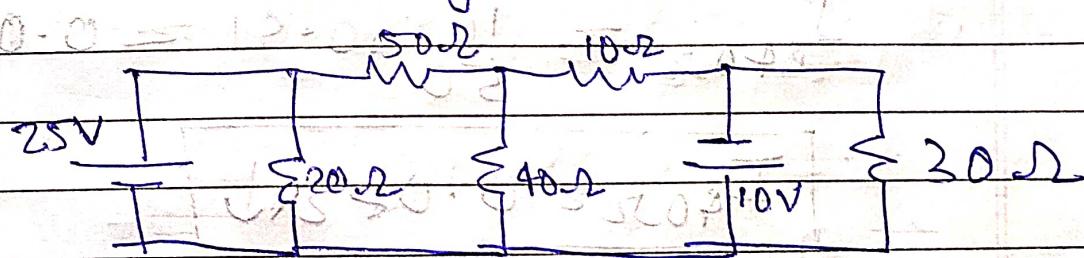- (7) Find the Current through 40Ωm resistor using Superposition Theorem



Taking (25V) battery

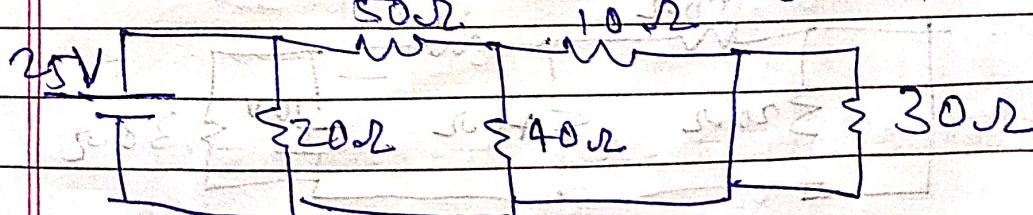

Since, there is short circuit-path

$$I_{30Ω} = 0$$

∴ R_{10} & R_{40} are in II

$$R = 8Ω$$

and in Series with R_{50}

$$25V \parallel \begin{cases} 20 \\ 58 \end{cases} R = \frac{[58 \times 20]}{58 + 20} \Omega$$

$$R = 14.87 \Omega$$

$$V = IR$$

$$I_T = 1.081 A$$


Now, by using Current division

$$I_{R_{20}} = 20 \times 1.081 = 0.41 A$$

$$I_{R_{40}} = \frac{10 \times 0.41}{50} = 0.082 A$$

$$I_{R_{30}} = 0.082 A$$

Case-II taking 10V battery

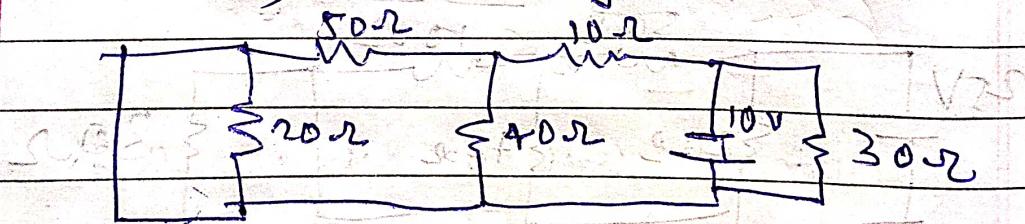

by R_{80} & R_{10} is Parallel

$$R = \frac{50 \times 40}{90} = 22.22 \Omega$$

$R_{(50||20)}$ & R_{10} is Series

$$R = 22.22 + 10 = 32.22 \Omega$$

by taking $R_{[(50||20)+10]\Omega}$ & $R_{30}\Omega$ in parallel

$$R = \frac{32.22 \times 30}{62.22} = 15.535 \Omega$$

$$\text{Total Current } (I_T) = \frac{250V}{15.535} = 0.64A$$

Now, by using Current division


$$I_{30} = \frac{30}{(32.22)\Omega} \times 0.64 = 0.31A$$

$$I_{40\Omega} = \frac{50}{62.22} \times 0.31 = 0.162A$$


$$\therefore \text{Net Current in } R_{40\Omega} = (0.162 - 0.082)A$$

$$I = 0.086A \uparrow$$

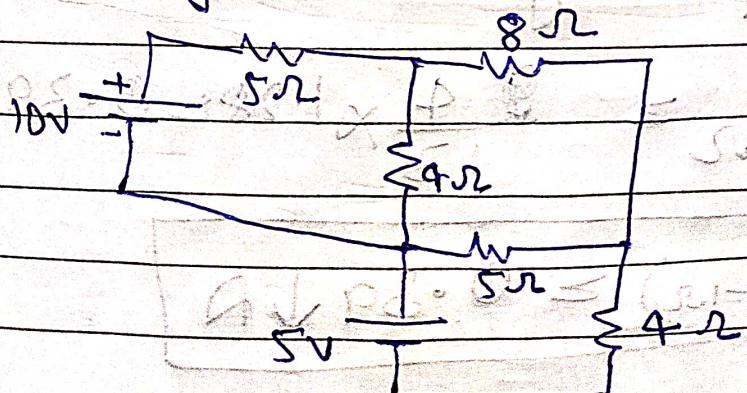Q.8 Find the Current through 1Ω using Superposition Theorem



Case-I, taking 10V battery

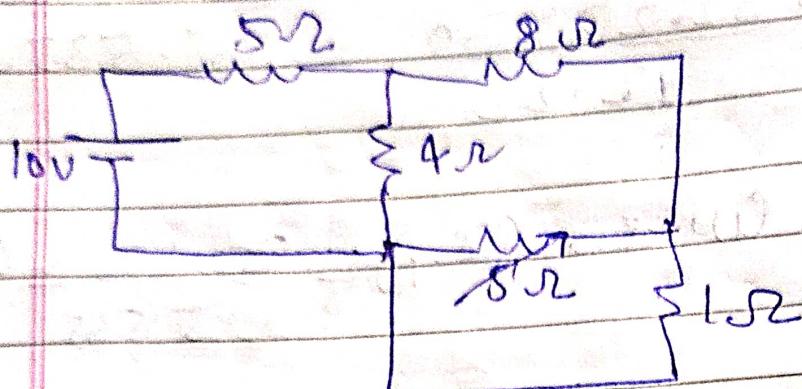

Here (R_{parallel}) will be short-circuited

R_i & R_g are in series

$$R_{\text{eq}} = 4 + 8 = 12 \Omega$$

$$R_{\text{eq}} = \frac{9 \times 4}{9 + 4} = 2.76 \Omega$$

& In series with R_{load}

$$R_{\text{net}} = 7.76 \Omega$$

$$I_{\text{Total}} = \frac{10}{7.76} = 1.28 \text{ A}$$


Now, by using Current division

$$I_{(8+1)\Omega} = \frac{4}{13} \times 1.28 = 0.39 \text{ A}$$

$$\therefore I_{(R=1\Omega)} = 0.39 \downarrow \text{A}$$

Case-II, taking 5V battery

Mayank Jothani
2012024

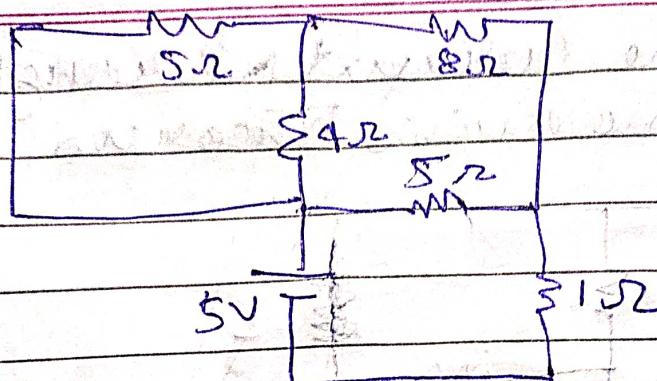

$R_{5\Omega}$ & $R_{4\Omega}$ are in Parallel

$$R = \frac{8 \times 4}{9} \approx 2.22\Omega$$

~~$$R = \frac{(5+4)\Omega \parallel (8\Omega)}{5+4}$$~~

$R_{15\Omega}$ & $R_{8\Omega}$ are in Series

$$R = 10.22\Omega$$

& $I_{15\Omega}$ is parallel with $R_{8\Omega}$

$$R = \frac{10.22 \times 5}{15.22} \approx 3.063\Omega$$

Total $R_{Net} \approx 4.63$

$$I_{Total} = \frac{5}{4.63} \approx 1.07A$$


$$(I_{R=1\Omega}) = 1.07 \downarrow A$$

$$\begin{aligned} \text{Total current in } 1\Omega &= (1.07 + 0.34) A \\ I &= 1.48 A \downarrow \end{aligned}$$

(Counter-clockwise direction)

Q.9 Find the Current in 2Ω Resistors
using Thevenin's Theorem
Replacing V_{th},

Ans. 9

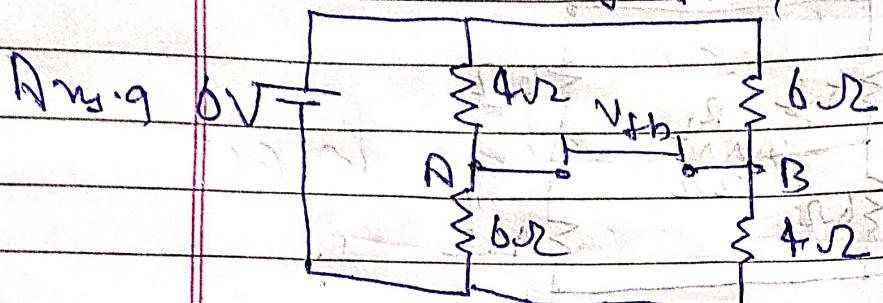


$R_{4\Omega}$ & $R_{6\Omega}$ are in series

$$R = 10\Omega$$

∴ Then the Thévenin $R_{10\Omega}$

$$R_{\text{net}} = \frac{10 \times 10}{10+10} = 5\Omega$$

$$\boxed{I = 6 \text{ A}}$$

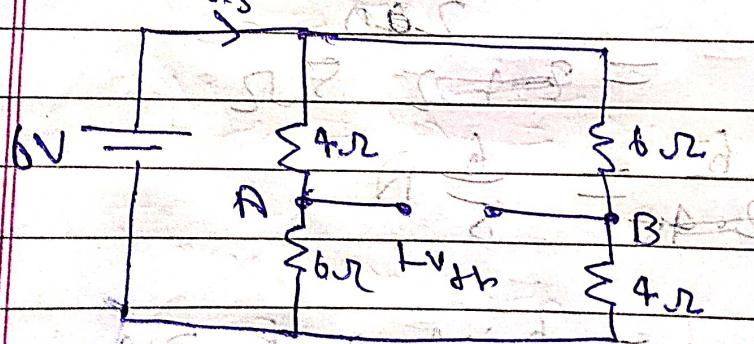

$$V_{DE} = 6 - 2 = 4 \text{ V}$$

by Current division

$$I_{4\Omega} = \frac{3}{5} \text{ A} \quad \& \quad I_{6\Omega} = \frac{3}{5} \text{ A}$$

$$V_D = 6 - \frac{3}{5}(4)$$

$$= 1.2 \text{ V}$$

Mayank Johari
2012024



Date _____
Page _____

$$V_B = 6 - \frac{6 \times 3}{5} = 1.2 \text{ V}$$

$$V_{th} = V_A - V_B = \frac{18}{5} - \frac{12}{5} = \frac{6}{5} \text{ V}$$

$$V_{th} = \frac{6}{5} \text{ Volts}$$

For find R_{th}

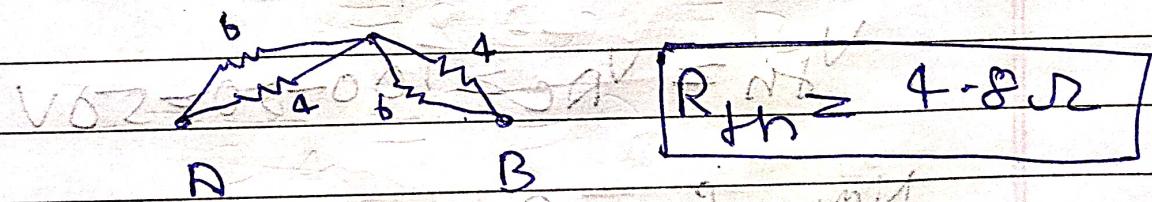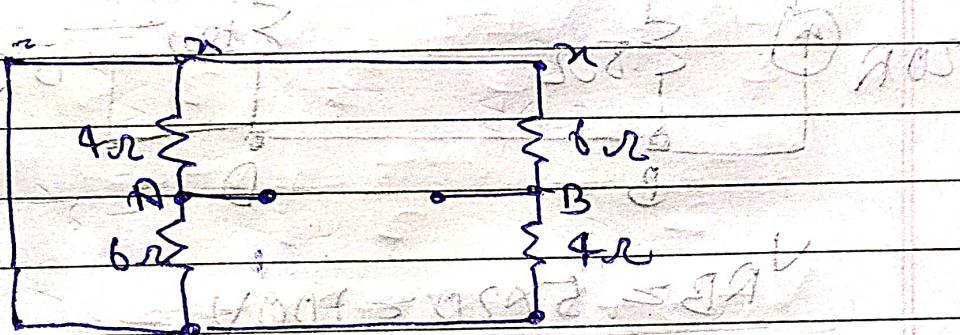

$$R_{th} = 4.8 \Omega$$

$$V_{th} = \frac{6}{5} \text{ V}$$

$$I_{2\Omega} = \frac{V_{th}}{R_{th} + R_L}$$


$$= 6$$

$$5 \times 6.8$$


$$= 0.12 \Omega$$

$$I_{2\Omega} = 0.126 \text{ A}$$

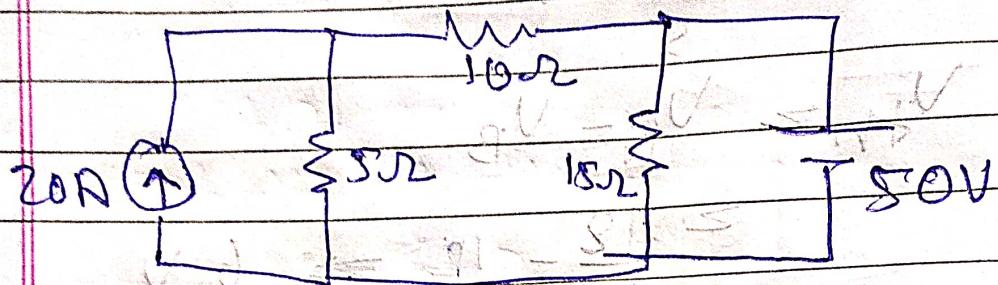Q10 Find the Current through 10Ω resistors
using Thevenin theorem



In order to find, V_{th}

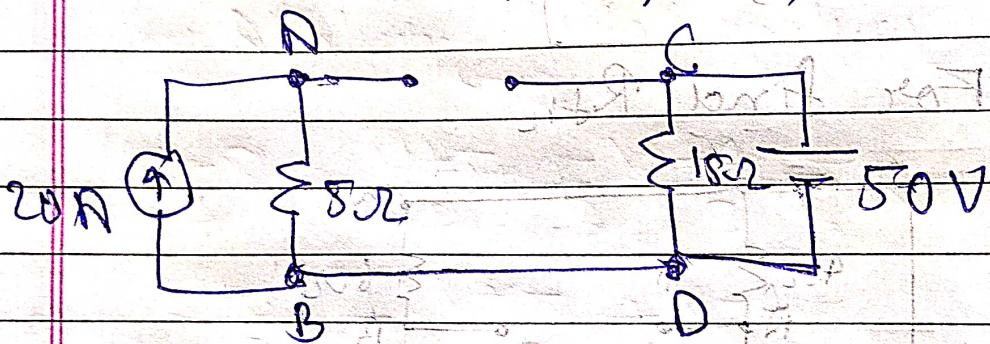


$$V_{NB} = 5 \times 20 = 100V$$


$$V_{CD} = 50$$

$$V_{th} = V_{AC} = 100 - 50 = 50V$$

Now, for R_{th}

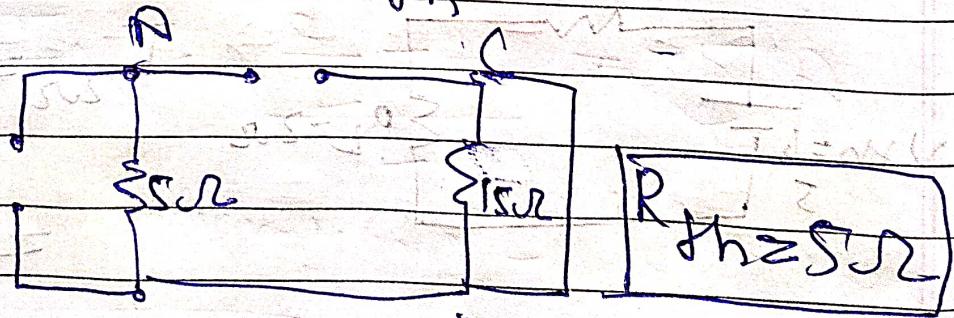


Now, the Thevenin Circuit looks like

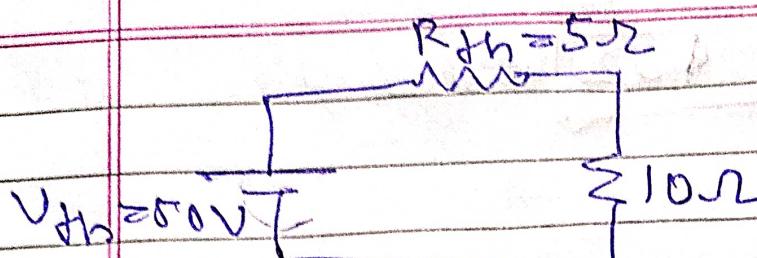


$$I = \frac{V_{Th}}{R_{Th} + 10} = \frac{50}{15} = 3.33$$

$$I_{10\Omega} = 3.33A$$

Q.11 Find the current in 6\Omega resistance using Norton's theorem.

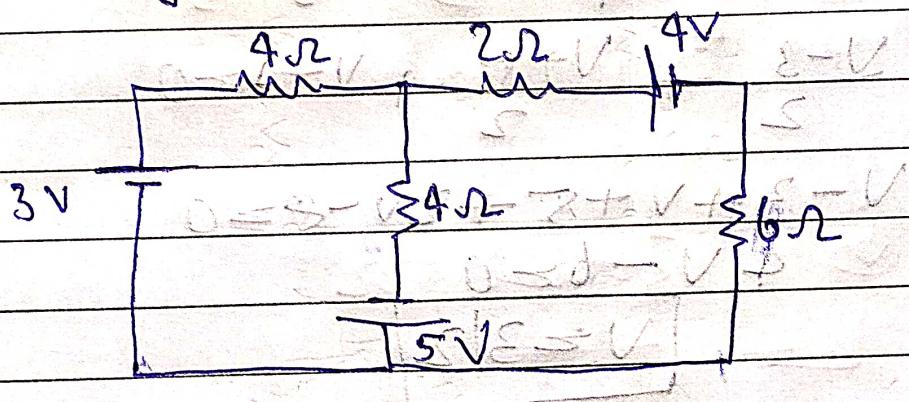

Avg. 11

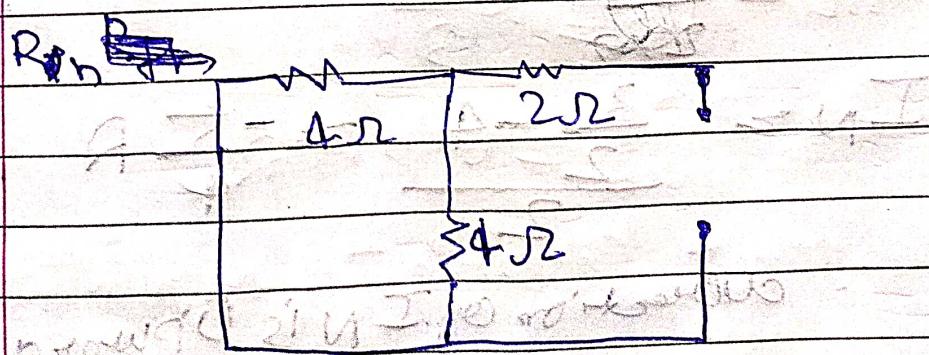

R_{AB} & R_{BC} in Parallel

$$R = 2\Omega$$


R_{BC} & R_{AB} are in Series

Mayank Toballi
20120824

Date _____
Page _____

$$TR_N = 4 \Omega$$

For I_N

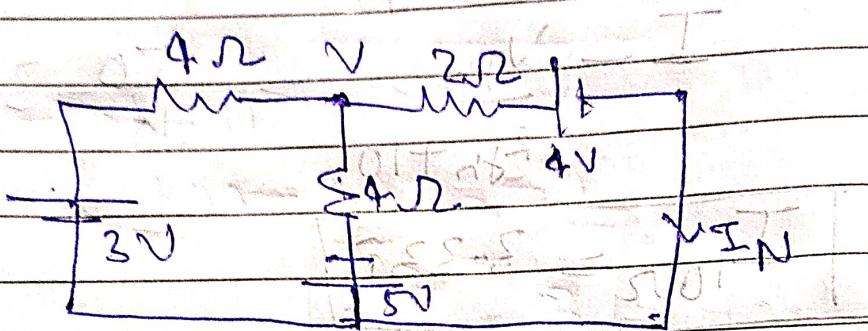

by Applying Nodal analysis

$$\frac{V-3}{4} + \frac{V+8}{4} + \frac{V-4}{2} = 0$$

$$\frac{V-3}{2} + \frac{V+8}{2} + V-4 = 0$$

$$V-3 + V+8 + 2V-8 = 0 \quad | \quad V \cancel{=}$$


$$4V - 6 = 0$$

$$V = 3/2$$

$$\frac{V-3}{1} = \frac{3}{2} - 4 = -\frac{5}{2}$$

$$I_N = \frac{3}{2} - 4 = -\frac{5}{2} A$$

∴ direction of I_N is Upward

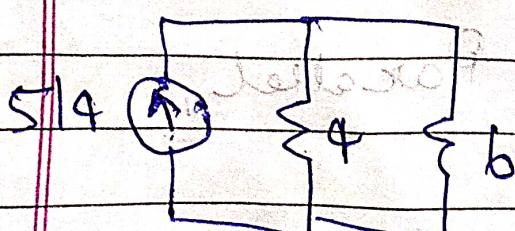

Mayank Jaiswal

2012024

Date _____
Page _____

Applying Current division


$$I_{B2} = \frac{A \times S}{10 + A} = \frac{1 \times 5}{10 + 1} = 0.5 \text{ A}$$

~~Ist~~


11 - 309 -

Current through R_2 is 0.5 A

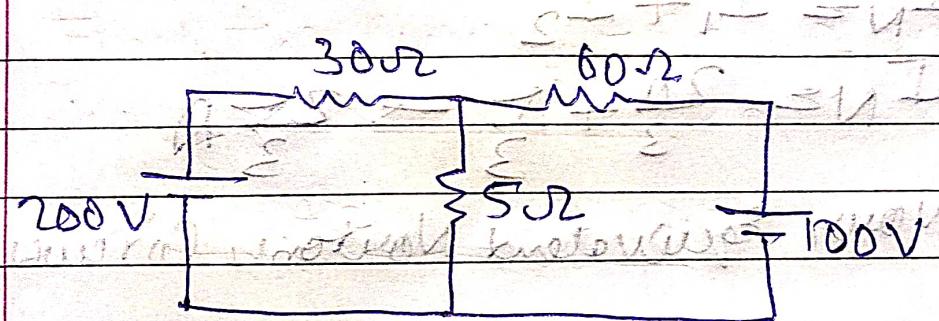Q.12 Find the current through using
Newton's theorem




Find R_N

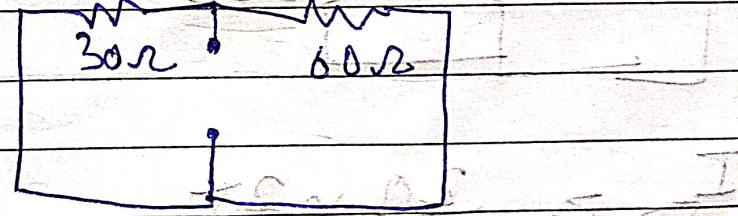

$$R_N = \frac{30 \times 60}{90} = 20 \Omega$$

$$R_N = 20 \Omega$$

Finding I_N

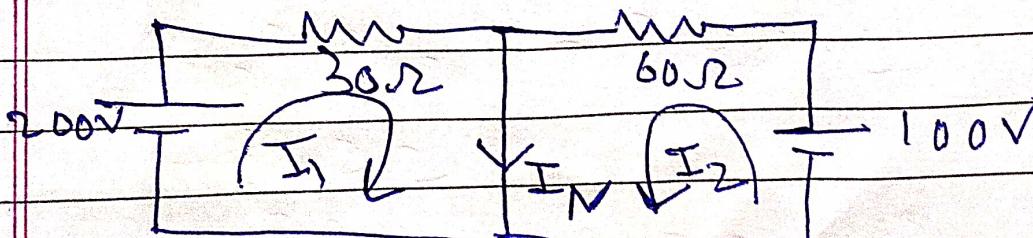

Mayank Toshniwal

2012024

Date _____
Page _____

by Applying KVL

Loop - I

$$200 - 30I_1 = 0$$

$$I_1 = 20/3$$

Loop - II


$$100 - 60I_2 = 0$$

$$I_2 = 5/3$$

$$I_N = I_1 + I_2$$

$$I_N = \frac{20}{3} + \frac{5}{3} = \frac{25}{3} A$$

Now Equivalent Norton's Circuit

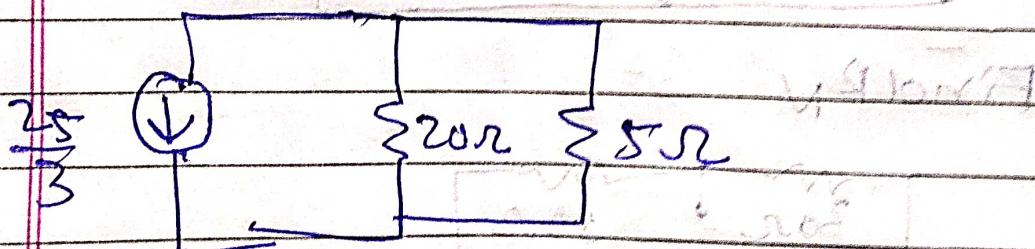

$$I_{SR} = \frac{20}{20+20} \times \frac{25}{3}$$

$$= \frac{25}{3} = 6.665 A$$

∴ Current through SR is 6.665 A.