

Rectifiers → AC voltage into pulsating DC converter



Half-Wave Rectifier:-

(i) Average or DC load current :-

$$I_{av} \text{ or } I_{dc} = \frac{I_m}{\pi} = 0.318 I_m \text{ (Ideal)}$$

(2) RMS or AC load current :-

$$I_{rms} = \frac{I_m}{2}$$

$$(3) V_{dc} = \frac{V_m}{\pi} = 0.318 (V_m) \text{ or } 0.318 (V_m - V_k)$$

Ideal Non-Ideal

$$(4) V_{rms} = \frac{V_m}{2}$$

$$(5) \text{ Ripple factor } (\gamma) = 1.21 = \sqrt{(F_F)^2 - 1} \quad (F_F = 1.57)$$

$$(6) \text{ Peak Inverse Voltage (PIV)} \geq V_m$$

$$(7) \% \eta = 90.51\% \quad \text{in case of half wave rectifier}$$

Full wave Rectifier:-

(A) Bridge Rectifier:-

$$(1) I_{dc} = \frac{2 I_m}{\pi} = 0.636 I_m \text{ or } 0.636 (V_m - 2V_k)$$

$$(2) V_{dc} = \frac{2 V_m}{\pi} = 0.636 V_m \text{ or } 0.636 (V_m - 2V_k)$$

(3)

$$I_{\text{rms}} = \frac{I_m}{\sqrt{2}}$$

$$V_{\text{rms}} = \frac{V_m}{\sqrt{2}}$$

(4)

$$\% \eta = 81.06\%$$

(5)

$$\gamma = 0.48$$

(6)

$$f_R = 2f_S$$

(7)

$$P \cdot I \cdot V \geq V_m$$

(B)

Center-Tapped Transformer :-

$$P \cdot I \cdot V \geq 2V_m$$

Zener Diode as Voltage Regulator

Case-I :- V_i & R_L are fixed

→ Calculate V_{Th} across the Zener diode.

→ (A) If $V_{Th} \geq V_Z \Rightarrow$ ON

$$V_{Th} = V_i \cdot \frac{R_L}{R_i + R_L}$$

(B) If $V_{Th} < V_Z \Rightarrow$ OFF

SubCase (A) Replace diode by equivalent battery of V_Z & use KCL & KVL to calculate all the values.

SubCase (B) Replace diode by open circuit & use KVL & KCL to calculate all the values.

Case-II - V_i fixed & R_L variable.

(i) Condition for min. load resistance (R_L) to activate Zener diode (ON) :-

$$\rightarrow \boxed{\text{Voltage across Z-D} = V_Z}$$

$$\checkmark R_{L\min} = \frac{V_Z \cdot R}{V_i - V_Z}$$

$$I_R = I_{Z\min} + I_{L\max}$$

$$\boxed{I_{L\max} = \frac{V_L}{R_{L\min}} = \frac{V_L}{R_{L\min}}}$$

$$\Rightarrow I_{Z\min} = I_R - I_{L\max} \\ = \frac{(V_i - V_Z)}{R} - I_{L\max}$$

(ii) Condition for max. R_L :-

$$R_{L\max} \Rightarrow I_{L\min} \Rightarrow I_{Z\max}$$

$$P_{Z\max} = I_{Z\max} \cdot V_Z \Rightarrow$$

$$\boxed{I_{Z\max} = \frac{P_{Z\max}}{V_Z}}$$

$$\checkmark \boxed{R_{L\max} = \frac{V_L - V_Z}{I_{L\min} / I_{Z\max}}}$$

$$\Rightarrow I_{L\min} = I_R - I_{Z\max} \\ = \frac{(V_i - V_Z)}{R} - \frac{P_{Z\max}}{V_Z}$$

Case-III V_i variable & R_L fixed

(i) Condition for min^m V_i :- $V_{th} \approx V_Z$

$$\Rightarrow \boxed{(V_i)_{\min} = \frac{V_Z (R + R_L)}{R_L}}$$



(ii) Condition for max. V_i :-

$(V_i)_{\max}$ is limited by $(I_z)_{\max}$.

$$I_R \max = I_z \max + I_L$$

$$\text{fixed } \left\{ \begin{array}{l} \therefore I_L = \frac{V_f - V_2}{R_L} = \frac{V_2}{R_L} \\ \text{fixed} \end{array} \right.$$

$$V_{i\max} = I_R \times R + V_2$$

case - IV

Both V_i & R_L variable
(Range of V_i is given & we have to calculate range of R_L)

$$R_{\min} = \frac{V_{i\max} - V_2}{I_R \max}$$

$$R_{\max} = \frac{V_{i\min} - V_2}{I_R \min}$$

$$I_R \geq I_z + I_L \Rightarrow \frac{V_i - V_2}{R} \geq I_z + I_L$$

Calculate R using eq. ② for limiting values of V_i & take the minimum value of R .

Common Emitter Configuration

→ C.E. configuration acts as Current Amplifier

$$\boxed{\beta = \frac{\alpha}{1-\alpha}}$$

$$I_C = \beta I_B + (\beta+1) I_{CBO}$$

$$\Rightarrow I_C = \beta I_B \quad (I_{CEO} \approx 0)$$

→ The contribution of leakage current in CE configuration is much ~~more~~ significant while in C.B. configuration, it is very low.

$$\boxed{\beta = \frac{I_C}{I_B}} \rightarrow \text{Amplification Factor}$$

$$(50 \leq \beta \leq 400)$$

i/p Current $\rightarrow I_B$
 i/p Voltage $\rightarrow V_{BE}$

o/p curr. $\Rightarrow I_C$
 o/p voltage $\Rightarrow V_{CE}$

<u>J₁</u>	<u>J₂</u>	<u>Region of Operation</u>
F·B	R·B	Active \longrightarrow Amplifier
F·B	F·B	Saturation \longrightarrow 'ON'
R·B	R·B	Cutoff \longrightarrow 'OFF'

Common - Base Configuration

$$\boxed{I_E = I_B + I_C} \quad ①$$

$$\boxed{I_C = \alpha I_E + I_{CBO}} \rightarrow \text{open circuit}$$

\hookrightarrow Reverse saturation current

$$\alpha = \frac{I_C}{I_E}$$

Common base current gain
Amplification Factor

$$0.95 \leq \alpha \leq 0.98$$


Input Characteristics (i_{p}/I vs i_{p}/V for diff values of op/V)

i/b T = L

$$\text{if } V = V_{BE}$$

$$0/b \quad I^+ - I_c$$

$$\text{off } V = V_{CB}$$

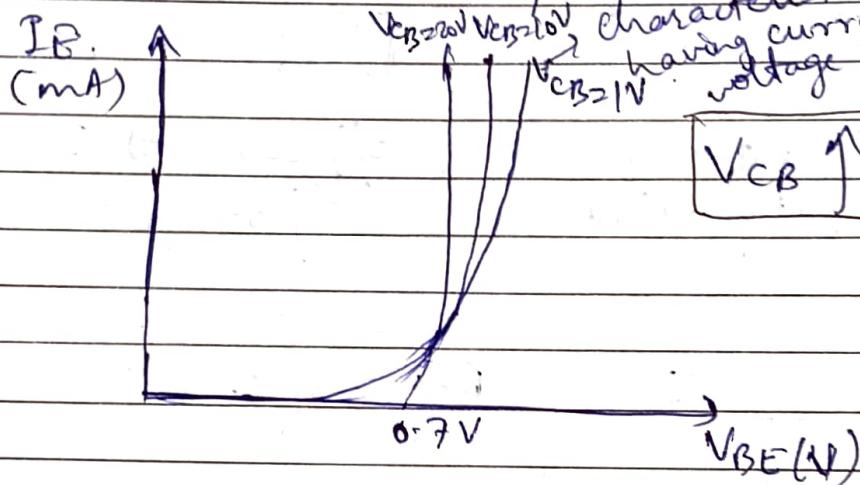


Output Characteristics

Plot of

\Rightarrow O/p I (I_C) vs O/p V (V_{CB}) for various levels of i/p I (I_E)

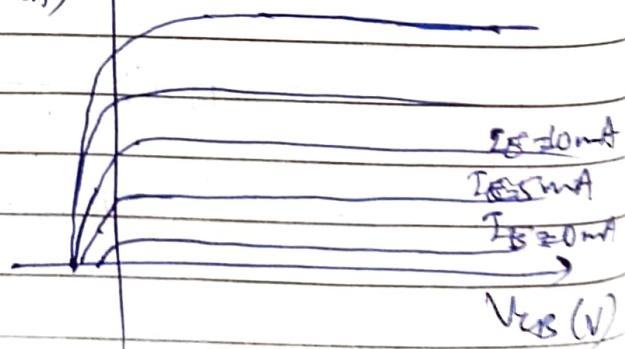
$\Rightarrow I_c$ is independent of V_{CB} &
 $I_c \approx I_E$



C-E Configuration


Input characteristics :

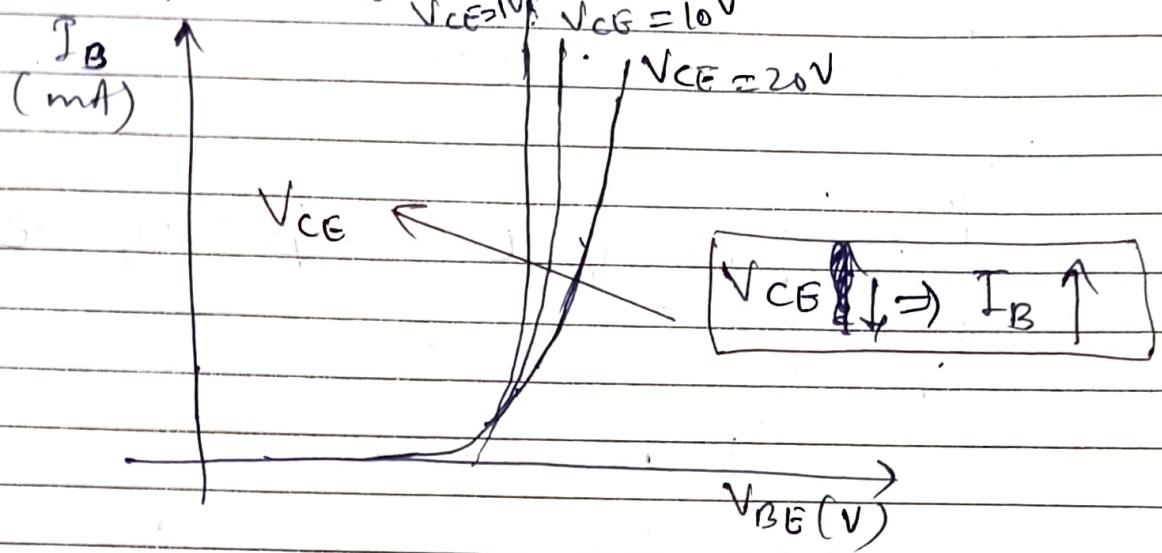→ i/p $I(B)$ Vs i/p $V(V_{BE})$ for diff values of output voltage (V_{CE})



Output Characteristics

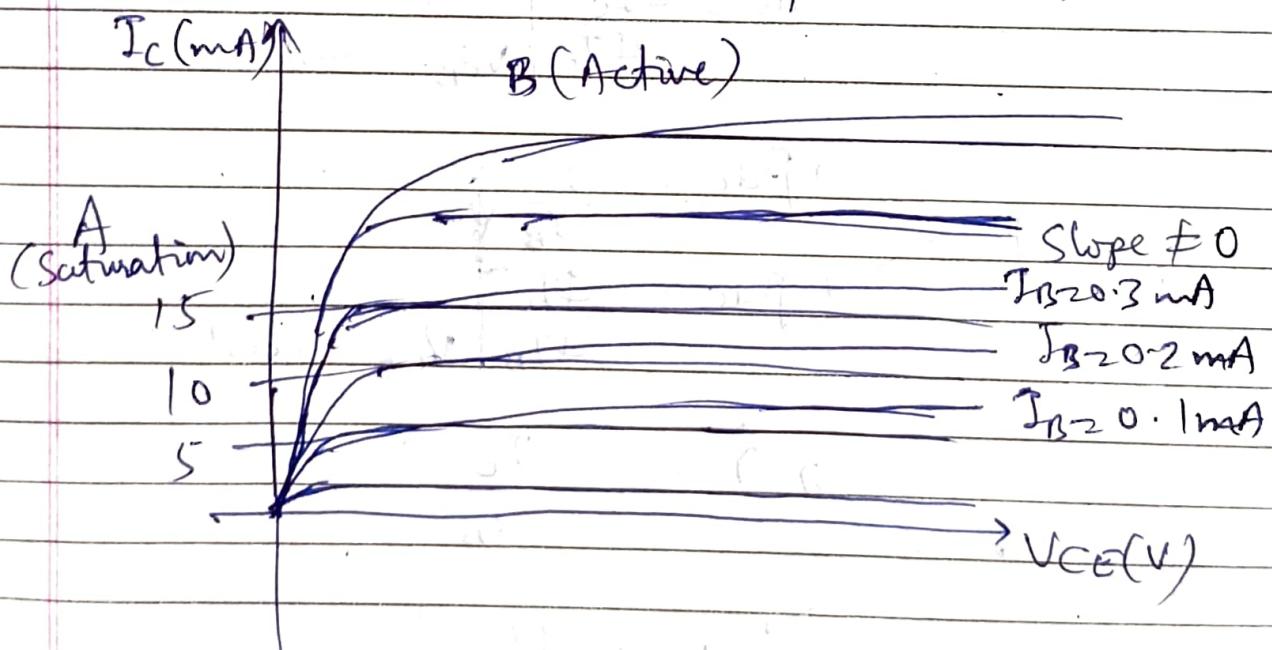Plot of o/p curr. (I_C) vs o/p voltage (V_{CE}) for diff. ~~no~~ levels of i/p curr. (I_B).



→ I_C is independent of V_{CE} & $I_C = (\beta + 1) I_{CBO}$

Common - Collector Configuration

Output characteristics

I_E vs V_{CE} for various levels of I_B

o/p current output voltage

$$I_E \approx I_C$$

↳ o/p ch. of C.C = o/p ch. of C.E.

$$\gamma = \frac{4I_E}{\Delta I_B}$$

Relation b/w α , β & γ

$$\alpha \rightarrow \alpha_{dc} = \frac{I_C}{I_E}$$

$$\alpha_{ac} = \frac{\Delta I_C}{4I_C} \quad | \quad V_{CE} = \text{const.}$$

output voltage

$$\beta \rightarrow \beta_{dc} = \frac{I_C}{I_B}$$

$$\beta_{ac} = \frac{\Delta I_C}{4I_B} \quad | \quad V_{CE} = \text{const}$$

$$\gamma \rightarrow \gamma_{dc} = \frac{I_E}{I_B}$$


$$\gamma_{ac} = \frac{\Delta I_E}{4I_B} \quad | \quad V_{CE} = \text{const}$$

$$2\beta + 1 = \frac{1}{1-\alpha}$$


$$\beta = \frac{\alpha}{1-\alpha}$$

$$\alpha = \frac{\beta}{1+\beta}$$


C-B \Rightarrow

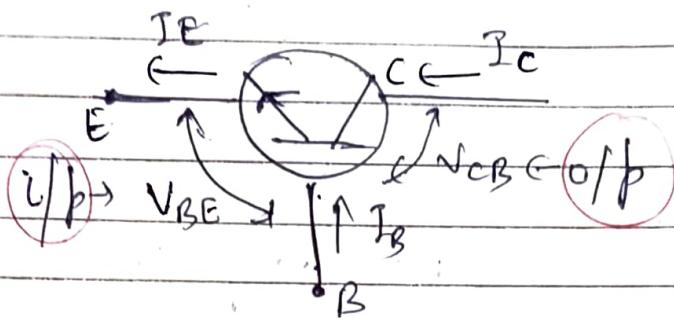

C-E \Rightarrow

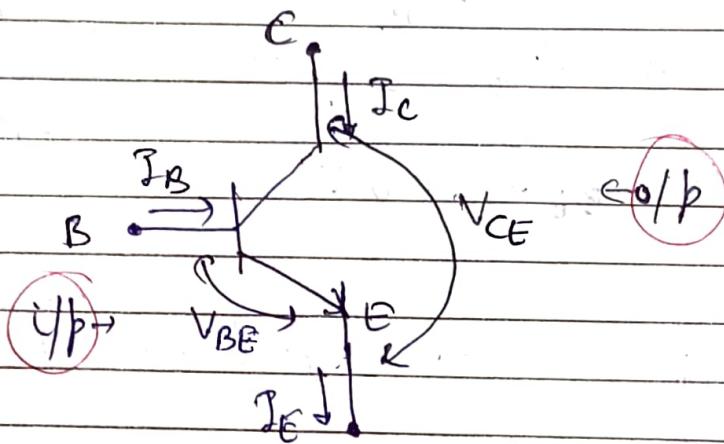

C-C \Rightarrow

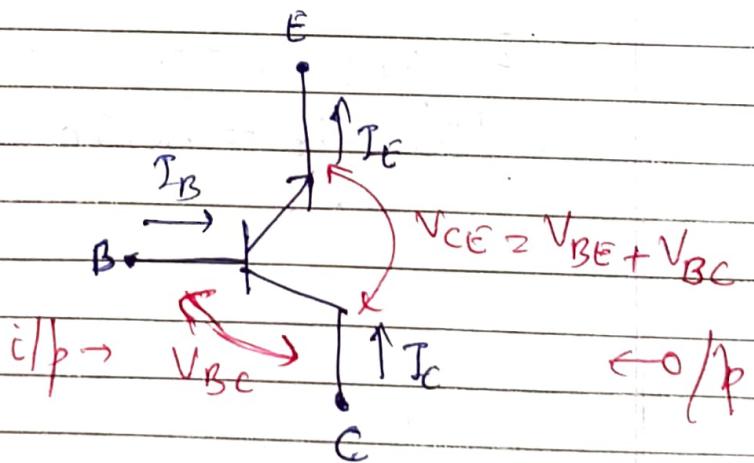

$$\beta = \frac{I_C}{I_B}$$

$$I_B \rightarrow I_C > \beta I_B \rightarrow V_{CE} \sim$$

Q pt (V_{CE}, I_C)
Operating pt.



(1)

Fixed - Bias Configuration
or Base - bias Configuration

→ Simply apply K.V.L using following points

$$I_C = \beta I_B$$

$$V_{BE} = \begin{cases} 0.7 \text{ V (for Si)} \\ 0.3 \text{ V (for Ge)} \end{cases}$$

(2)

Emitter - Bias Configuration

→ Simply apply K.V.L using following points

$$(i) I_C = \beta I_B$$

$$I_E = I_B + I_C \\ = I_B + \beta I_B$$

$$(ii) I_E \approx I_C$$

$$(iii) V_{BE} = 0.7 \text{ V (for Si)}$$


$$\Rightarrow I_E = (\beta + 1) I_B$$

(3) Collector - Feedback Biasing —


$$① I = I_B + I_C$$

$$② V_{BE} = 0.7 \text{ V}$$


$$③ I_E = I_B + I_C \approx I_C$$

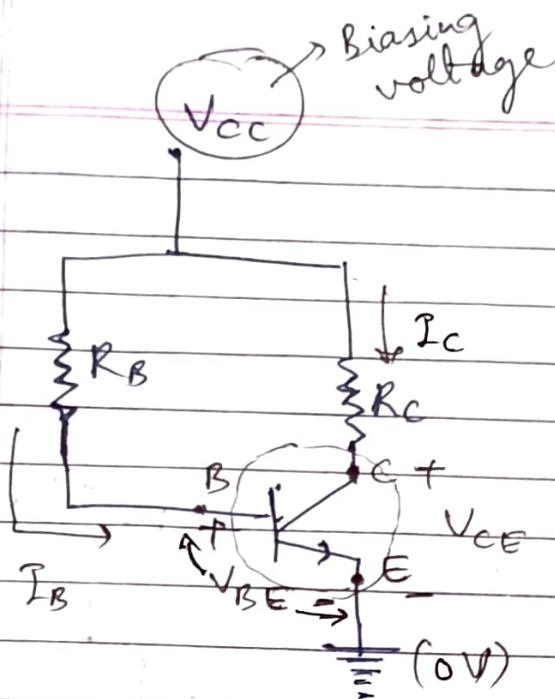

Fixed - bias Configuration

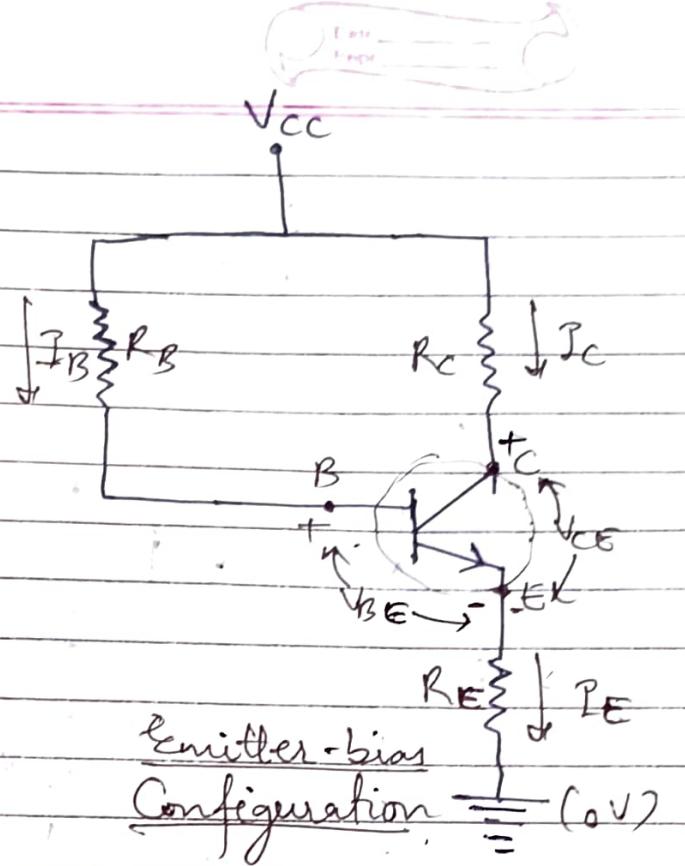


Emitter - bias Configuration

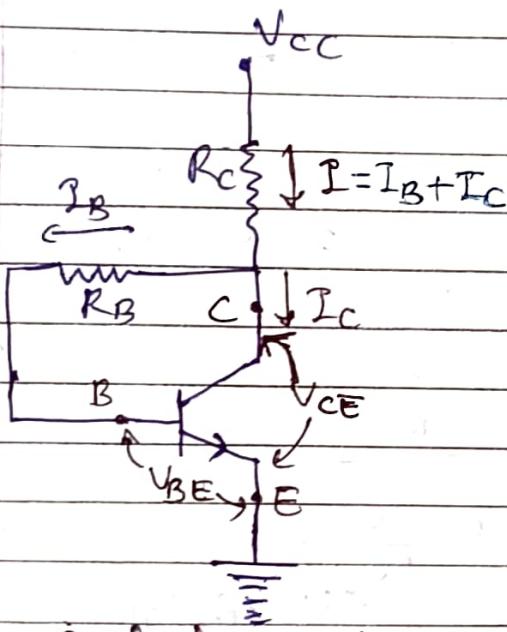

Collector - Feedback biasing


Voltage-Divider Configuration

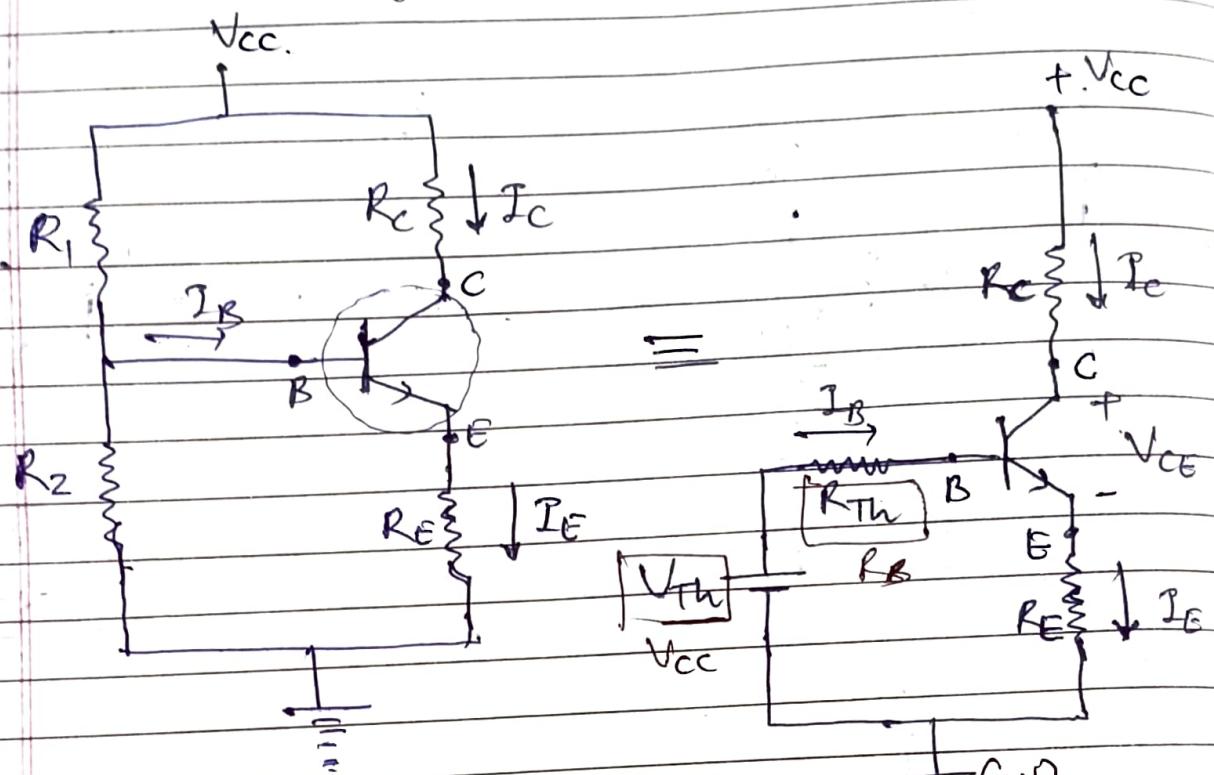

$$R_{Th} = \frac{R_1 R_2}{R_1 + R_2}$$

Similar to -emitter-
-bias config.
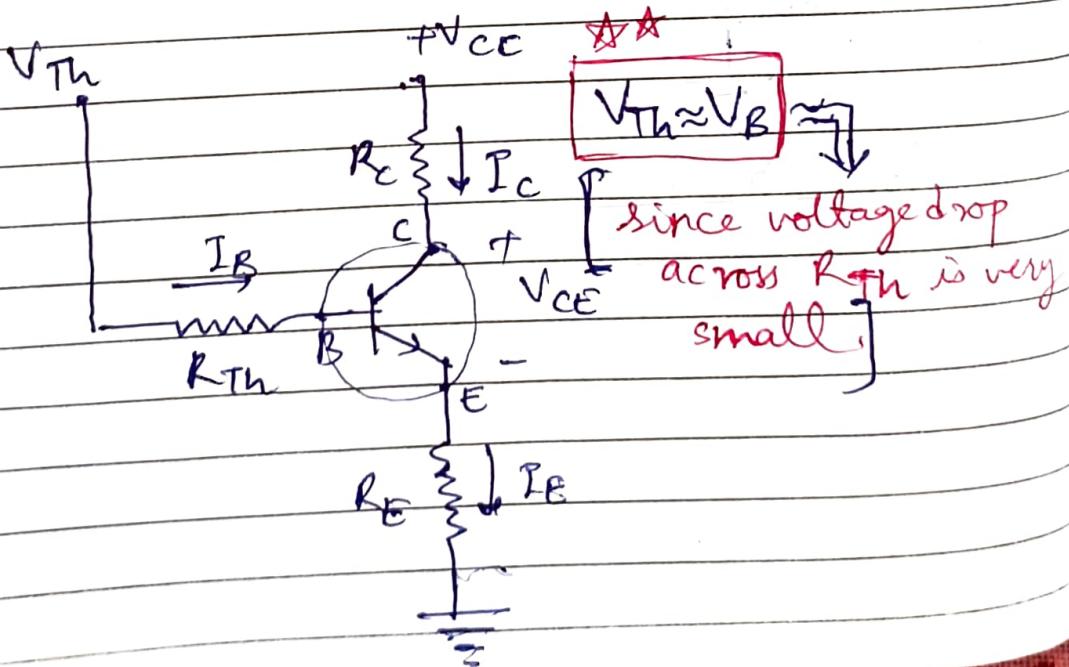
$$V_{Th} = I R_2 = \frac{R_2 V_{cc}}{R_1 + R_2}$$



n-channel Enhancement - Type MOSFET

$V_{GS} \uparrow \Rightarrow$ width of ch \uparrow

$$V_{GD} = V_{GS} - V_{DS}$$

Case-I :- $V_{DS} = 0 \Rightarrow V_{GD} = V_{GS} \Rightarrow$ uniform d.R.

Width of channel is corresponding to the excess voltage.

$$\text{Excess voltage} = V_{GS} - V_T$$

$V_T \rightarrow$ given

Case-II :- $V_{DS} > 0 \Rightarrow V_{GD} \downarrow \Rightarrow D$ becomes more flat
 \Rightarrow Channel D.R. on D side \uparrow due to \uparrow in r.b
 \Rightarrow Channel width becomes narrower on D-side

Case-II :- $V_{DS} = V_{GS} - V_T$ \rightarrow Pinch-off condition
 $\Rightarrow V_{GD} = V_T$

o/p i $\rightarrow I_D$
 o/p v $\rightarrow V_{DS}$

Controlling Variable = V_{GS}

If $V_{DS} = 0 \Rightarrow V_D = V_S \Rightarrow I_D = 0$

For Saturation Region :- $V_{DS} \geq V_{GS} - V_T$

If $V_{DS} = V_{DS\text{sat.}} \Rightarrow (I_D = \text{const.})$ (Pinch-off)

$$I_D = k(V_{GS} - V_T)^2$$

const. \leftarrow given


$$k = \frac{I_D(\text{on})}{(V_{GS(\text{on})} - V_T)^2} \text{ A/V}^2$$

$$V_{GS} \downarrow \Rightarrow S \downarrow \Rightarrow R \uparrow \Rightarrow \text{Slope of Drain ch.} \downarrow$$

(∴ Slope $\propto \frac{1}{R}$)

For Triode Region :- $V_{DS} < V_{GS} - V_T$
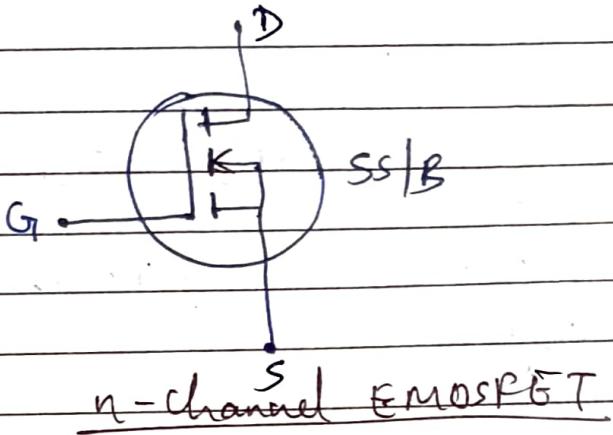
$$I_D = 2k_s \left[(V_{GS} - V_T) V_{DS} - \frac{V_{DS}^2}{2} \right]$$



n-channel Depletion - Type MOSFET
Working \approx n-channel JFET

JFET

$$\rightarrow V_{GS} > 0$$


$$\rightarrow V_{GS} \leq 0$$

$\rightarrow I_{DSS}$ is the max^m transistor current
& I_{DS0} is the current

$$I_D \text{ corr. to } V_{GS} = 0$$

DMOSFET


$$V_{GS} = 0$$

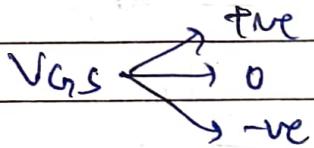

\rightarrow Current corr. to $V_{GS} > 0$ is I_{DS0} but it is not max^m current

V_{GS} more +ve $\Rightarrow I_D$ rapid
 V_{GS} more -ve $\Rightarrow I_D \downarrow$

When $V_{GS} = V_p \Rightarrow I_D = 0$

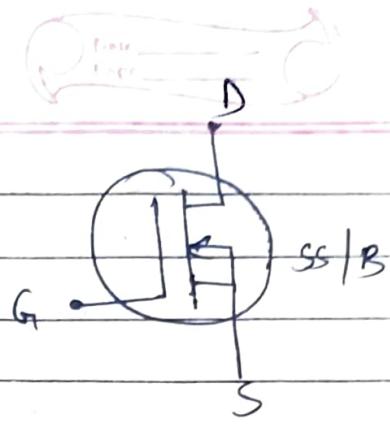


JFET (n-channel)

$\rightarrow I_G > 0$ always due to r.b

Case-I: $V_{GS} > 0$ V

Case II r $\textcircled{G} V_{GS} < 0$

$$V_{DS} > 0$$

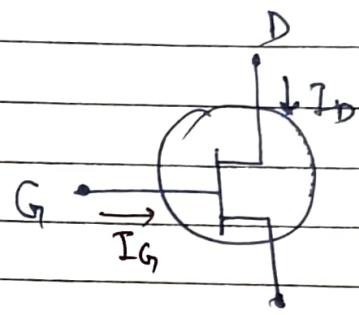

Pinch-off Condition :-

Two D-Rs seem to touch each other.

When $|V_{DS}| > |V_p|$

$I_D = I_{SS} = \text{const}$ \rightarrow max current

JFET acts as a constant-current source

When $V_{GS} < 0$:- We obtain the sat. at lower value of V_{DS}

o/p $i \rightarrow I_D$ for various controlling $V \rightarrow V_{GS}$
o/p $V \rightarrow V_{DS}$

Drain ch.

→ In ohmic region, JFET can be used as Voltage-controlled Resistor i.e. Var. Resistance

$$\text{Slope} = f(V_{GS}) \quad \& \quad V_{GS} \downarrow \Rightarrow \text{Slope} \downarrow \Rightarrow R \uparrow$$

Resistance at $V_{GS}=0$

$$r_d = \frac{r_0}{\left(1 - \frac{V_{GS}}{V_p}\right)^2}$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_p}\right)^2 \quad (\text{Non-linear})$$

const.

$$\rightarrow \text{when } V_{GS} = V_p \Rightarrow I_D = 0 \quad \checkmark$$

$$\rightarrow \text{When } V_{GS} = 0 \text{ V} \Rightarrow I_D = I_{DSS}$$

Transfer ch. :-

$$\text{if } I \rightarrow I_D \quad \text{Vs} \quad \text{if } V \rightarrow V_{GS}$$

$$\text{for const. if } V \rightarrow V_{DS}$$