

Network Analysis And Synthesis

circuit :- A closed path for current to flow

network :- may or may not be closed

* Every circuit is a network but not vice-versa.

→ Various Net Terms.

1) Circuit : A conducting path through which an electric current either flows or is intended to flow, is called a circuit.

2) Linear circuit : A circuit whose parameters are constant or which obey Ohm's law is called linear circuit.

3) Non-linear circuit : A circuit whose parameters change with voltage or current or which does not obey Ohm's law, is called non-linear circuit.

* KVL \Rightarrow No. of eqn = No. of loopsKCL \Rightarrow No. of eqn = Nodes - 1

4) Unilateral circuit: A circuit whose properties or characteristics change with the direction of voltage or current, is called unilateral circuit.

5) Bilateral circuit: A circuit whose properties or characteristics remains same in either dir'n is called bilateral circuit.

6) Active circuit: A circuit which contains one or more than one source of EMF is called an Active circuit.

7) Passive circuit: A circuit which does not contain any source of EMF is called passive circuit.

8) Node: A node is a junction in a circuit where two or more circuit elements are connected together.

9) Branch: The part of a network which lies between two junctions is called a branch.

Types of sources :-

i) Independent Source.

ii) Voltage

iii) Current

ii) Dependent Source :


i) VDVS

ii) VDCS



iii) CDVS

iv) CPCS



ideal voltage source.

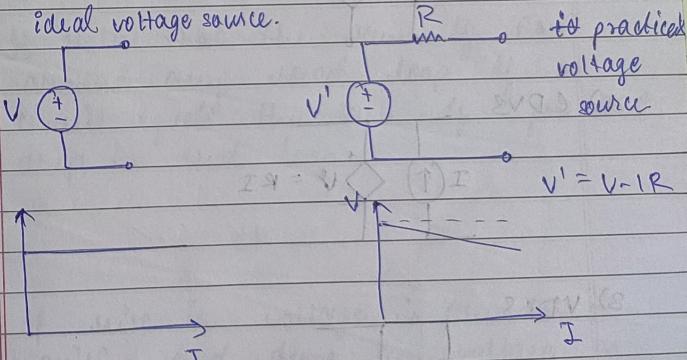


ideal current source

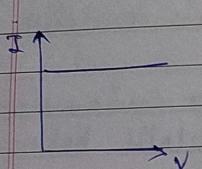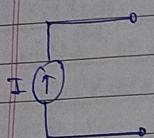


practical current source

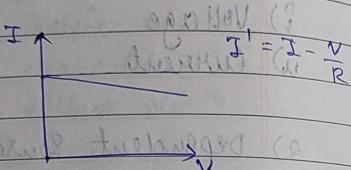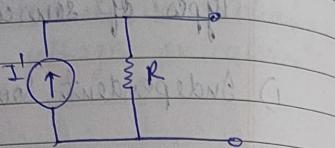


1) VDVS

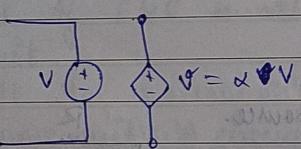


2) CDVS

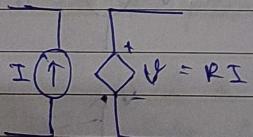


3) VDCS

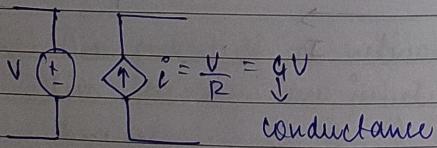

4) CDCS

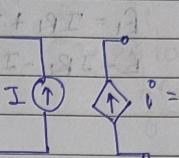

Voltage-Current source conversion:

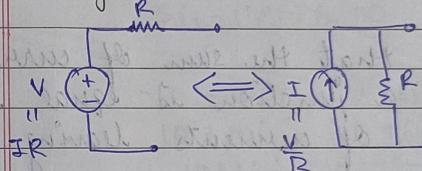


KVL

It states that the sum of EMF around any closed loop of a circuit equals the sum of potential drop in that loop.

OR

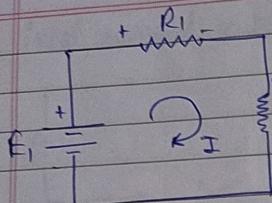If rise in voltage is considered positive and drop in voltage as negative, then the algebraic sum of potential diff. around a closed loop is 0.



$$E_1 = I R_1 + i R_2$$


$$E - i R_1 - I R_2 = 0$$

KCL

It states that the sum of currents entering a junction is equal to the sum of currents leaving the junction.

OR.

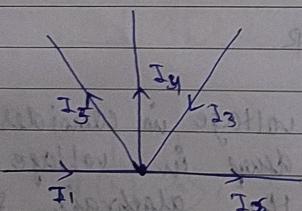
If the currents towards the junction is considered the and those away as -ve then the algebraic sum of all currents meeting at a common junction is 0



$$I_1 + I_3 = I_2 + I_4 + I_5$$

$$I_1 + I_3 - I_2 - I_4 - I_5 = 0$$

(Q1)

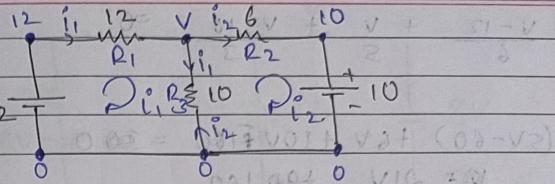

$$V_{12} - 12i_1 - 10(i_1 - i_2) = 0$$

$$12 - 22i_1 + 10i_2 = 0$$

$$5i_2 - 11i_1 + 6 = 0 \quad \text{--- (1)}$$

$$-10 - 10(i_2 - i_1) - 6i_2 = 0$$

$$10 + 10(i_2 - i_1) + 6i_2 = 0$$

$$10 + 16i_2 - 10i_1 = 0$$

$$5 + 8i_2 - 5i_1 = 0 \quad \text{--- (2)}$$


$$i_1 = +0.36 \text{ A}$$

$$i_2 = -0.39 \text{ A}$$

$$V_1 = 0.36 \times 12 = 4.32 \text{ V}$$

$$V_2 = 0.39 \times 6 = 2.34 \text{ V}$$
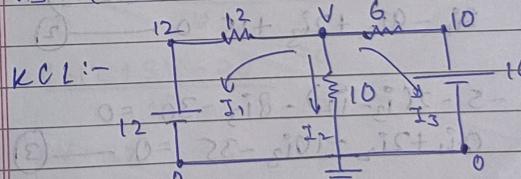
$$V_3 = (0.36 + 0.39) \times 10 = 7.5 \text{ V}$$



$$I_1 + I_2 + I_3 = 0$$

$$\frac{V-12}{12} + \frac{V-0}{10} + \frac{V-10}{6} = 0$$


$$\frac{V-12}{6} + \frac{V}{5} + \frac{V-10}{3} = 0$$

$$(5V-60) + 6V + 10V - 100 = 0$$

$$10V = 160$$

$$V = 16V$$

$$Q_1 = (V = 16V, i_1 = 1A, i_2 = 1A)$$

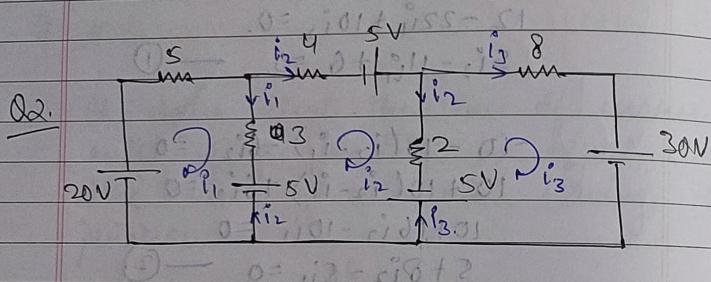

Solve by Mesh analysis.

$$KVL: 20 - 5i_1 - 3(i_1 - i_2) - 5 = 0 \Rightarrow i_1 = 3$$

$$15 - 8i_1 + 3i_2 = 0$$

$$-8i_1 + 3i_2 + 15 = 0 + 0i_3 + 15 = 0 \quad (1)$$

$$V_{UDS} = 2 \times 15 = 30V$$

$$5 - 3(i_2 - i_1) - 4i_2 + 5 - 2(i_2 - i_3) + 5 = 0$$

$$3i_1 - 9i_2 + 2i_3 + 15 = 0 \quad (2)$$

$$-5 - 2(i_3 - i_2) - 8i_3 - 30 = 0$$


$$0i_1 + 2i_2 - 10i_3 - 35 = 0 \quad (3)$$

$$i_1 = 2.55$$


$$i_2 = 1.82$$

$$i_3 = -3.13$$

Q3.

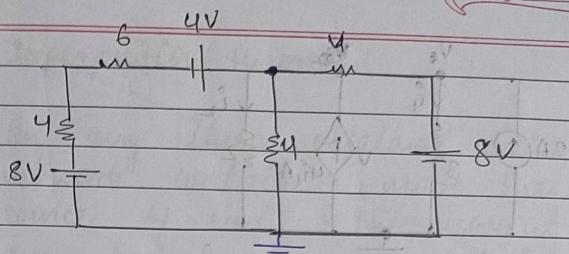

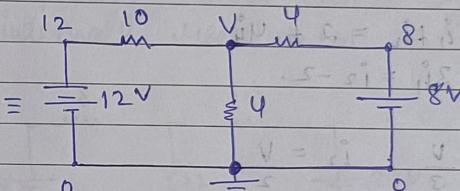Find i through 8Ω resistor using nodal voltage method.



$$\frac{V-12}{10} + \frac{V}{4} + \frac{V-8}{4} = 0$$

$$\frac{V-12}{10} + \frac{2V-8}{4} = 0$$

$$\frac{V-12}{10} + \frac{2(V-4)}{4} = 0$$

$$\frac{V-12 + 5V - 20}{10} = 0$$

$$6V = 32$$


$$V = \frac{32}{6} = \frac{16}{3}$$

$$V = 5.33V$$

$$i = \frac{5.33 - 12}{10}$$

$$= 0.667A$$

Q4

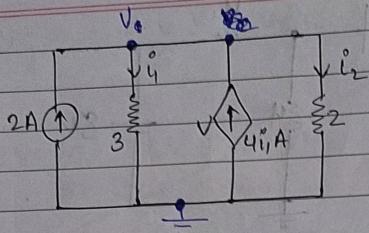

~~BY KIRCHHOFF'S LAW~~

$$-2 + \frac{V}{3} + \frac{V}{2} = 10$$

KCL: $i_1 + i_2 = 2 + 4$

$$3i_1 = i_2 - 2$$

$$i_1 = \frac{V}{3}, \quad i_2 = \frac{V}{2}$$

$$\frac{8-V}{3} = \frac{V-2}{2}$$

$$\frac{V}{2} = -2 \Rightarrow V = -4$$

$$i_1 = \frac{-4}{3} A, \quad i_2 = -2 A$$

$$0 = 2 \times (V - V) + 51 - V$$

$$0 = 0 - V + 51 - V$$

$$52 = V$$

$$i_1 = \frac{52 - V}{3}$$


$$51 - 52 = -1$$

$$V = 52$$


$$A.P.O.$$

Superposition theorem


In any linear bilateral active network containing more than one source of emf, the current in any branch is the algebraic sum of a no. of individual currents considering the emf separately, replacing other sources by their internal resistances.

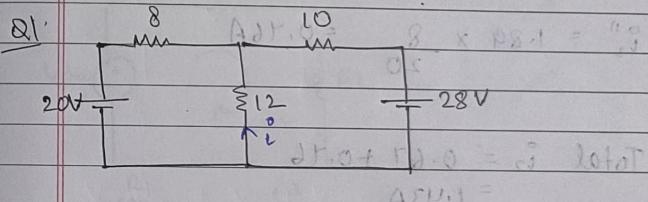

Considering 20V :-

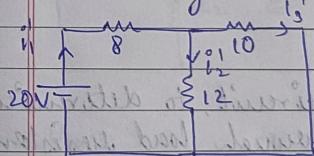

Considering 28V :-

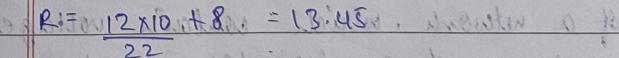


$R = 12 \times 10 / 22 = 13.45 \Omega$, smaller & $I = 22$

$i_1 = 1.48$ & $i_2 = 1.48$ (as in both cases 13.45Ω is common)

$i_1 = 1.48 \times 10 / 22 = 0.67 A$ (smaller)

$i_2 = 1.48 \times 10 / 12 = 1.23 A$ (larger)

considering 28V source:

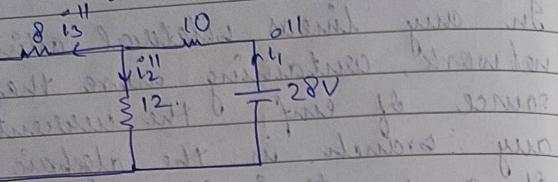

$$R = \frac{8 \times 12}{20} + 10 = 14.8 \Omega$$

$$I_1'' = \frac{V}{R} = \frac{8}{12} = 0.67 A$$




$$I_2'' = 1.89 \times \frac{8}{20} = 0.76 A$$

$$\text{Total } I_2 = 0.67 + 0.76 = 1.43 A$$

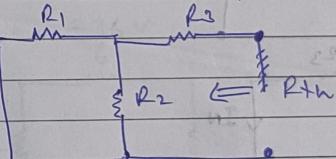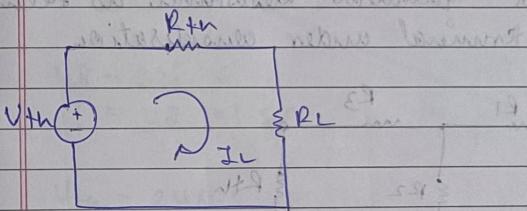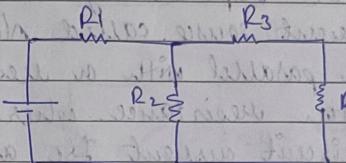3) Thevenin's Theorem

In any linear circuit, to determine the current through load resistor R_L , connected across two terminal of a network, which contains voltage sources and a resistor can be replaced by a single source of emf, called Thevenin's voltage V_{th} and a series resistor called Thevenin's resistance R_{th} , where V_{th} is the potential diff.

when R_L is removed and R_{th} is the equivalent resistance as seen from the terminal under consideration.




$$V_{th} = \frac{R_2}{R_1 + R_2} \times V$$

$$R_{th} = \frac{R_1 R_2}{R_1 + R_2}$$

$$I_L = \frac{V_{th}}{R_{th} + R_L}$$


u) Norton's Theorem

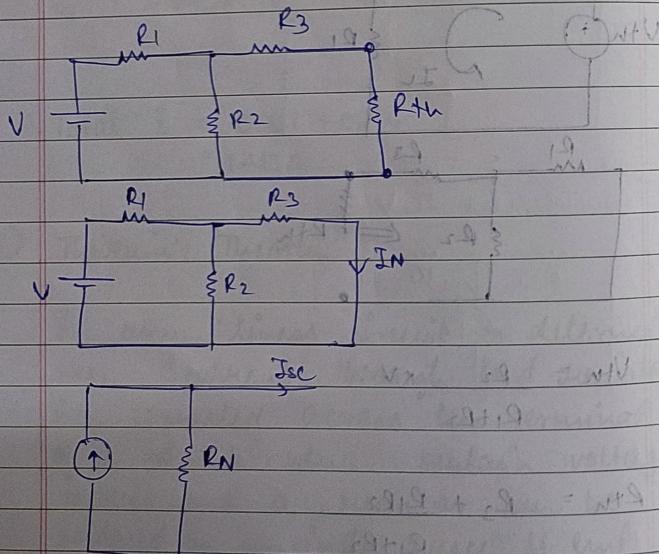In any linear network containing independent voltage and current sources may be replaced by an equivalent current source, called Norton current I_N in parallel with a resistance R_N called Norton resistance, where I_N is the short circuit current I_{SC} and R_N is equivalent resistance as seen from the terminal under consideration.




$$I_L = \frac{R_N}{R_N + R_L} \cdot I_N$$

Q1:

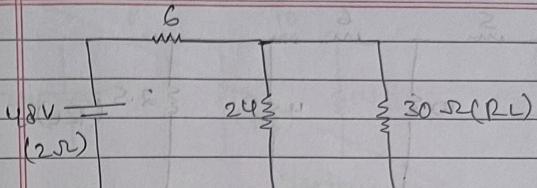

Thevenin's

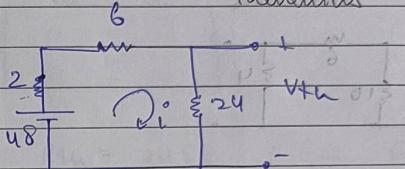


$$48 - 32i = 0$$

$$i = \frac{48}{32} = 1.5 \text{ A}$$


$$V_{TH} = 24 \times 1.5 = 36 \text{ V}$$

$$= 36 \text{ V}$$

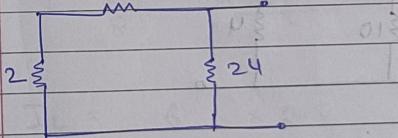


$$R_{TH} = \frac{24 \times 2}{32} = 6 \Omega$$
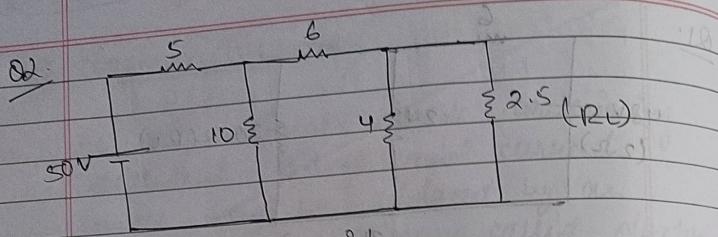
$$I_L = \frac{V_{TH}}{R_{TH} + R_L} = \frac{36}{6 + 30} = 1 \text{ A}$$



Thevenin's

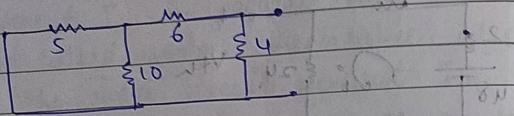


$$\frac{10 \times 5}{18} = \frac{10}{3} + 6 = 28$$

$$3i = 18 - 8N$$

$$R_{TH} = \frac{28 \times 4}{3} = 37.33 = 2.8$$


$$\frac{28+4}{3} = 13.33$$

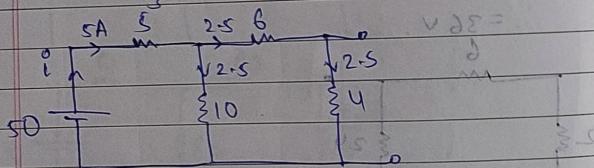


$$i = \frac{50}{10} = 5A$$

$$V_{RN} = 2.5 \times 4 = 10V$$


$$I_L = \frac{10}{2.8 + 2.5} = 1.88A$$

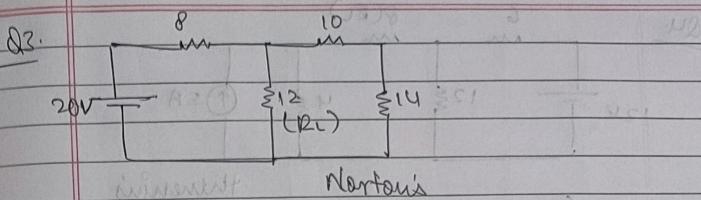

Equivalent Norton's

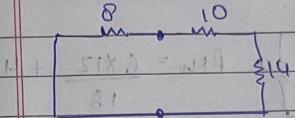
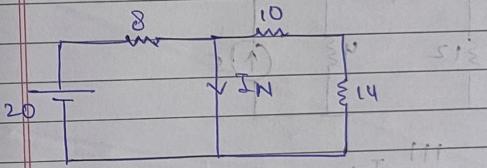
$$R_{TH} = \frac{20 \times 8}{20 + 8} = 6\Omega = R_N$$




$$i = \frac{20}{8} = 2.5A = IN$$





$$I_L = \frac{6}{6 + 12} \times 2.5$$

$$= 0.83A$$


Q4.

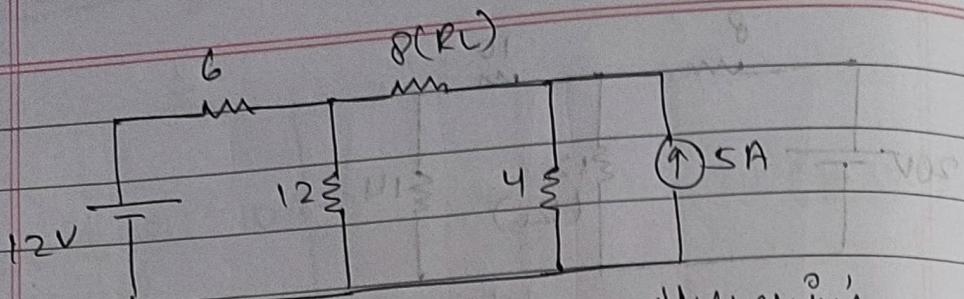


Thenevin's

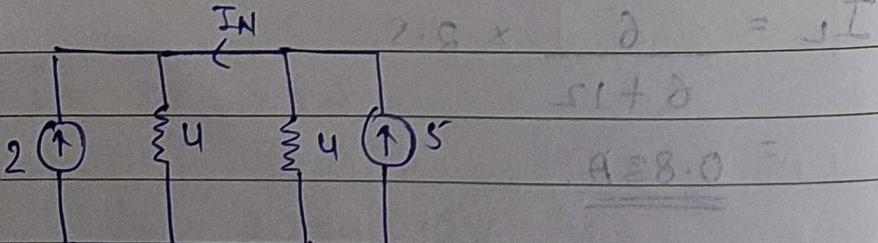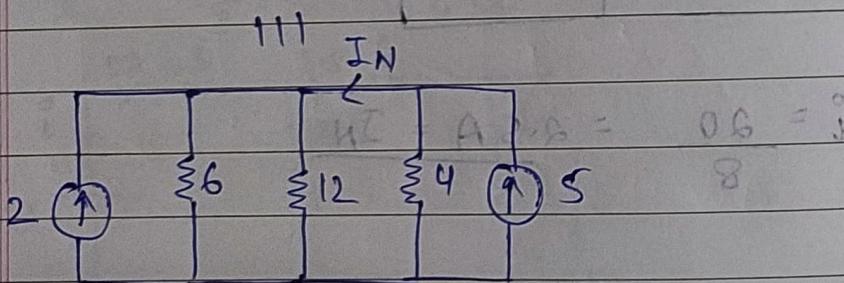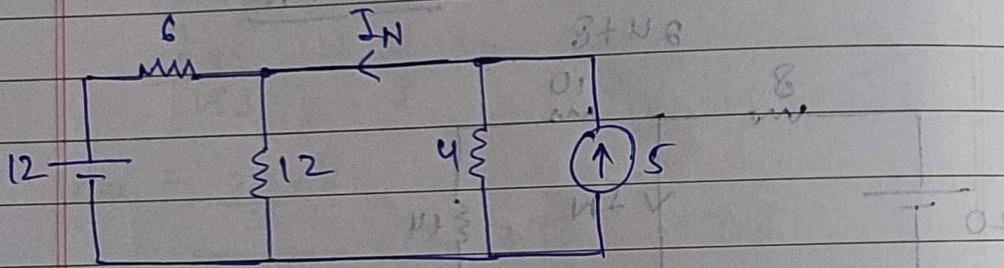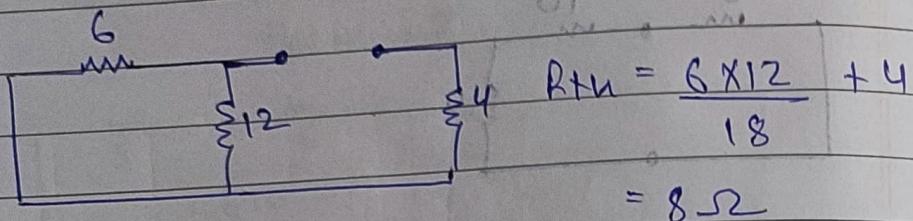

Q5.

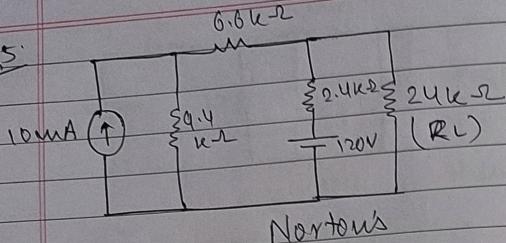


Norton's

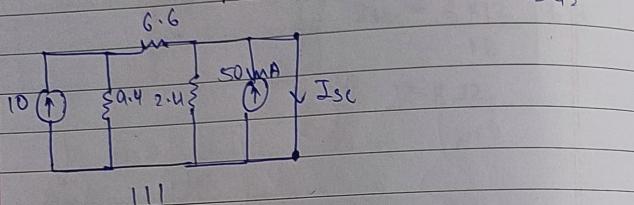


111

when 10mA current source works:

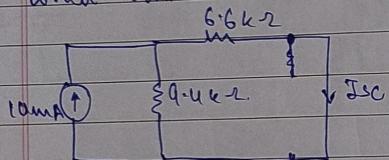


$$I_{sc_1} = 10 \times \frac{9.4}{16} = 5.875 \text{ mA}$$

when 50mA works:-

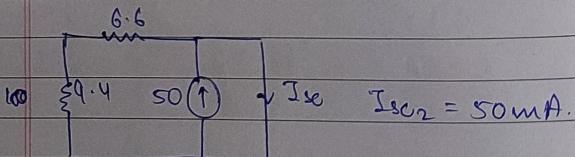

$$I_{sc} = I_{sc_1} + I_{sc_2}$$

$$= 55.875 \text{ mA}$$

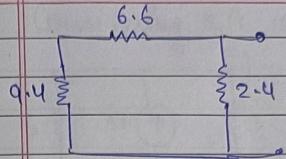

$$R_{th} = 16 \times 2.4$$




$$18.84$$

$$V_{1.1} = 2.087 \text{ } \cancel{\text{k}\Omega}$$


$$I_L = I_N \frac{R_{th}}{R_{th} + R_L}$$

$$= 55.875 \times \frac{2.087}{26.087}$$

$$= 4.44 \text{ mA}$$

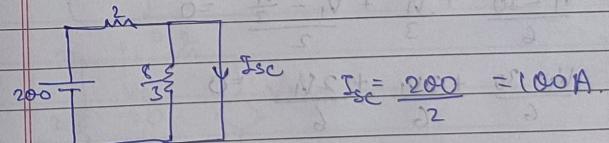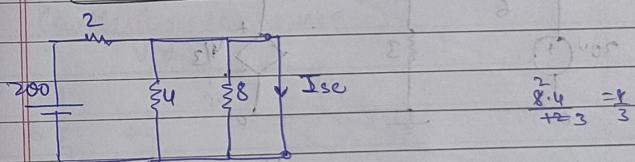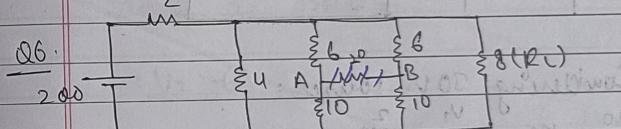

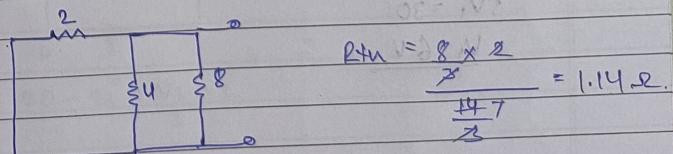
$$I_{sc} = \frac{200}{12} = 100 \text{ A}$$




$$R_{th} = \frac{8 \times 2}{\frac{14}{2}} = 1.14 \text{ } \cancel{\text{\Omega}}$$

$$I_L = I_{SC} \cdot \frac{R_{TH}}{R_{TH} + R_L}$$

$$= \frac{1.14}{0.12 + 1.14} = 12.5$$

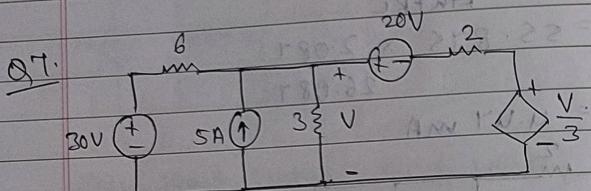

Considering 30V source:

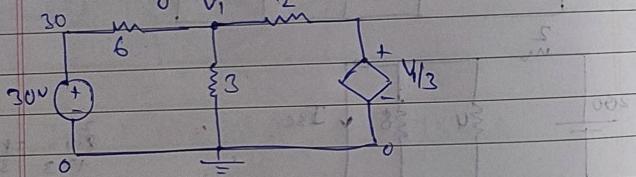



$$\frac{V_1 - 30}{6} + \frac{V_1}{3} + \frac{V_1 - V_1/3}{2} = 0$$

$$\frac{V_1 - 30}{6} + \frac{2V_1}{6} + \frac{2V_1}{6} = 0$$

$$5V_1 = 30$$

$$V_1 = 6V$$



Considering 20V source:

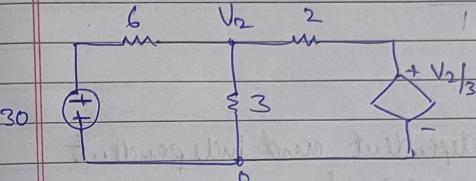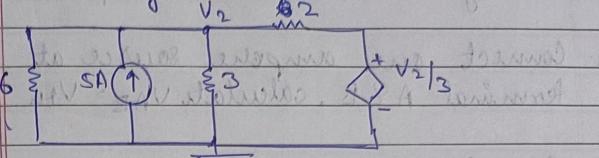

Same as previous

Hence $V_2 = 6V$. This is same as previous

Considering 20V source:-

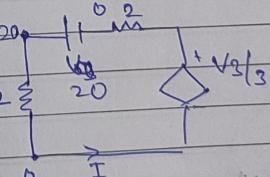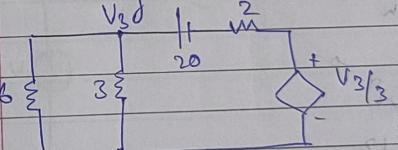

$$20 - 2i + \frac{V_3}{3} + 2$$

* If only dependent source is present


1. Connect one ammeter source at terminal A & B, calculate $V_{AB} = V_{th}$

$$2. R_{th} = \frac{V_{AB}}{I}$$

* If both dependent and independent source is present

1. Find V_{th} across AB
2. For R_{th} , short circuit AB and find I_{th} , then R_{th}

$$3. R_{th} = \frac{V_{th}}{I_{th}}$$

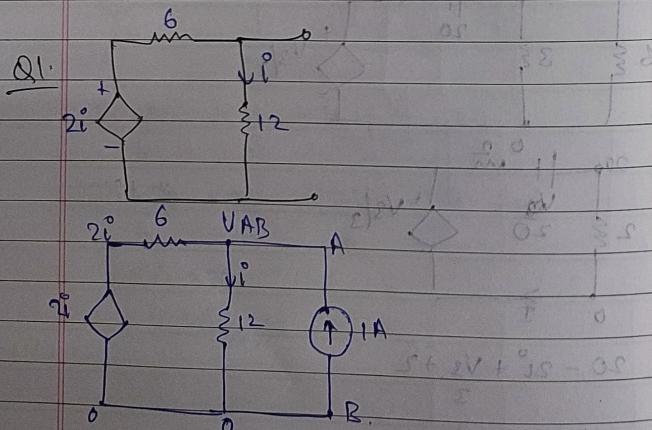

$$\frac{V_{AB}-2i}{6} + \frac{V_{AB}}{12} = 1$$

$$i = \frac{V_{AB}}{12}$$


$$\Rightarrow \frac{V_{AB} - V_{AB}}{6} + \frac{V_{AB}}{12} = 1$$

$$\frac{8V_{AB}}{36} + \frac{3V_{AB}}{36} = 1$$

$$8V_{AB} = 36$$



$$V_{AB} = \frac{36}{8} = 4.5V$$

$$R_{th} = V_{AB} = 4.5\Omega$$

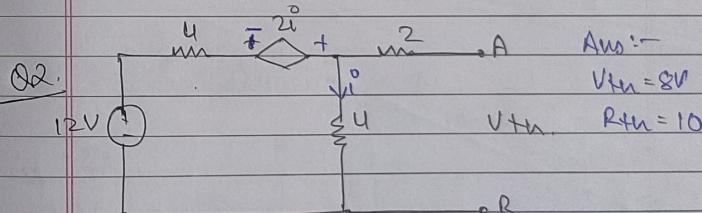


V Max Power Transfer Theorem

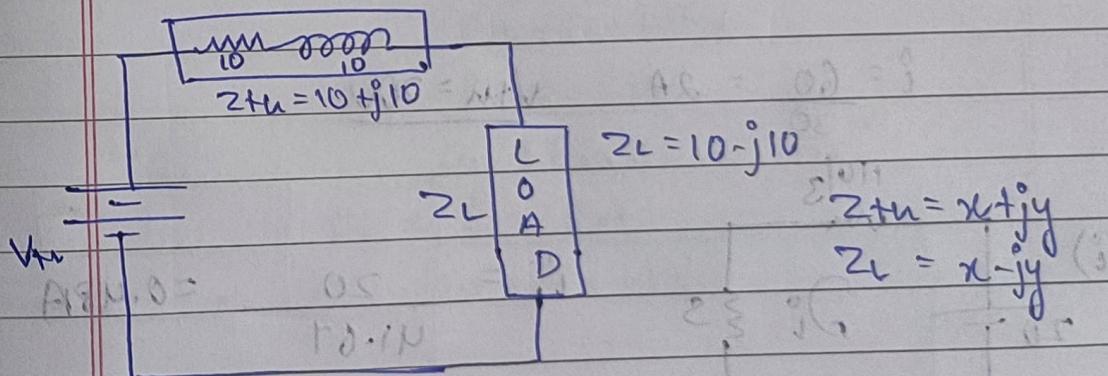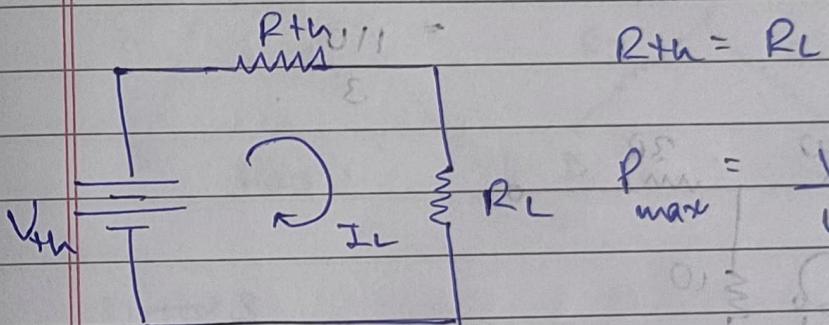It states that max power output is obtained from a network when the load resistance is equal to the output resistance of the network as seen from the terminals of the load.




$$Z_{th} = 10 - j10$$

$$25 \angle -90^\circ$$

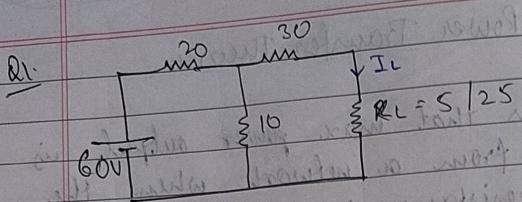


Cal value of R_L for which power is max.
Find this max power.
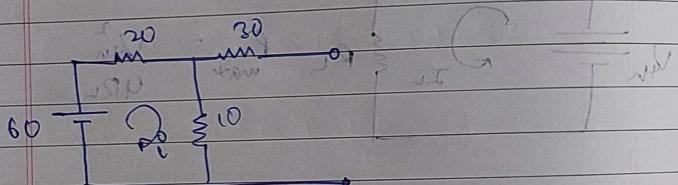
$$R_{Th} = 30 + \frac{20 \cdot 10}{30} = \frac{110}{3} \Omega$$




$$I = \frac{60}{30} = 2A$$

$$V_{Th} = 20V$$

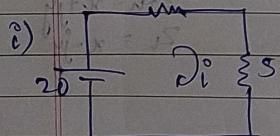

$$i_1 = \frac{20}{41.67} = 0.48A$$

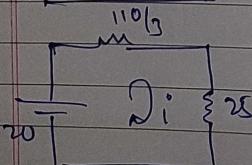



$$i_2 = \frac{20}{41.67} = 0.324$$

For max power, $R_{Th} = R_L = 36.67$

$$P_{max} = \frac{400}{4 \times 36.67} = 2.12W$$

VI

Star delta transformation

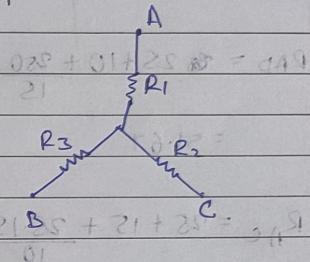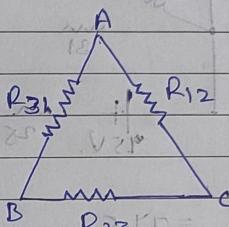

$$0.28 + 0.128 = 0.417$$

$$0.28 + 0.128 + 0.128 = 0.536$$

$$D \rightarrow S, \quad 0.21 + 0.1 + 0.1 = 0.42$$

$$R_1 = \frac{0.21}{R_{12} R_{31}}$$

$$R_{12} + R_{23} + R_{31} =$$

$$R_2 = R_{12} + R_{23}$$

$$R_{12} + R_{23} + R_{31}$$

$$R_3 = \frac{R_{23} \cdot R_{31}}{R_{12} + R_{23} + R_{31}}$$

$$S \rightarrow D, \quad R_{12} = R_1 R_2 + R_2 R_3 + R_3 R_1$$

$$= R_1 + R_2 + \frac{R_1 R_2 R_3}{R_1 R_2 + R_2 R_3 + R_3 R_1}$$

$$= 20.0 =$$


721/06

classmate


Date _____

Page _____

Q1.


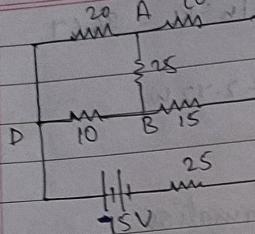

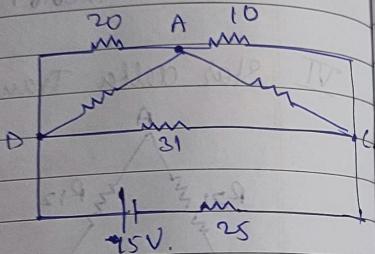
$$R_{AD} = \frac{25 + 10 + 250}{15} = 51.67$$



$$R_{AC} = 25 + 15 + \frac{25 \cdot 15}{10} = 77.5$$

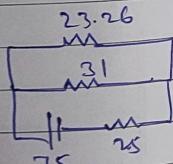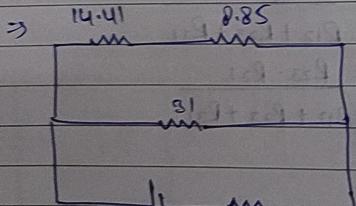
$$R_{CD} = 10 + 15 + \frac{150}{25} = 31$$



$$i = \frac{15}{38.28 \cdot 15.78} = -0.391A$$

$$= 0.95$$

Q2.

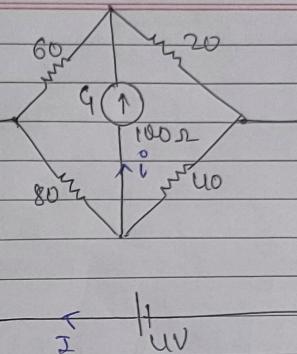


$$R_{eq} = 47.9$$

$$I = 0.083$$

$$i = 2.36 \text{ mA}$$

$40 + j50$

Q.

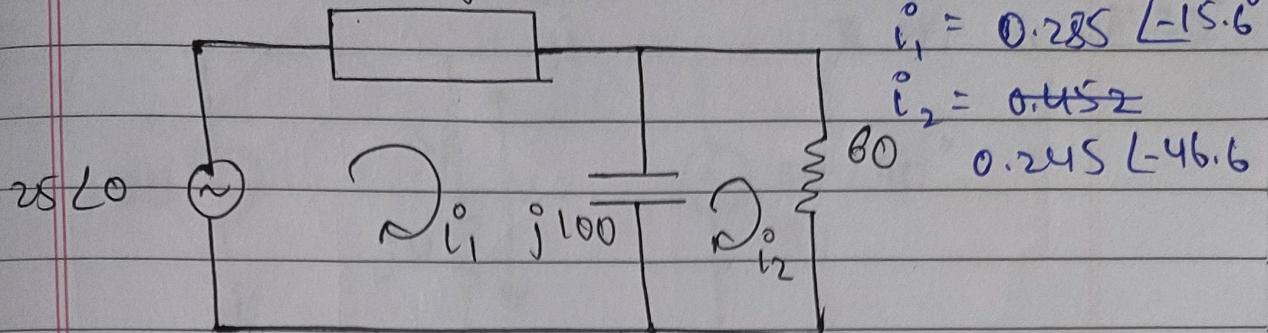

$$i_1 = 0.285 \angle -15.6^\circ$$

$$i_2 = 0.452$$

$$0.245 \angle -46.6^\circ$$

$$(40 - j50)i_1 + j100i_2 = 25\angle 0^\circ$$

$$+j100i_2 + (80 - j100)i_2 = 0$$

Polar form : $M\angle\theta$

Rectangular form :

$$M = \sqrt{x^2 + y^2}$$

$$\theta = \tan^{-1}\left(\frac{y}{x}\right)$$

$+, - \rightarrow$ Rect

$\times, \div \rightarrow$ Polar.



$$\text{eg: } \frac{10\angle 30^\circ}{5\angle 20^\circ}$$

$$= 2\angle 20^\circ$$

$$10\angle 30^\circ \times 5\angle 10^\circ$$

$$= 50\angle 40^\circ$$


Q4.

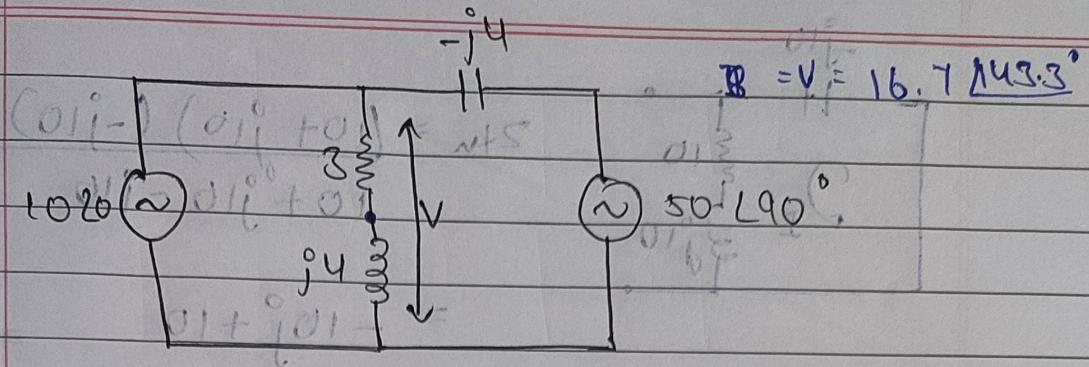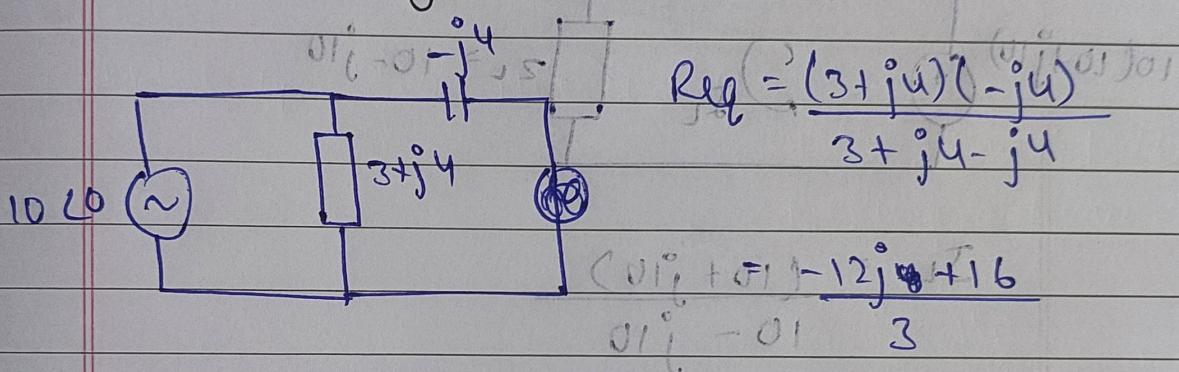for V Solve, using superposⁿ theorem


$$I = \frac{10 \angle 20^\circ}{\text{Req}}$$

Req.

Q5.

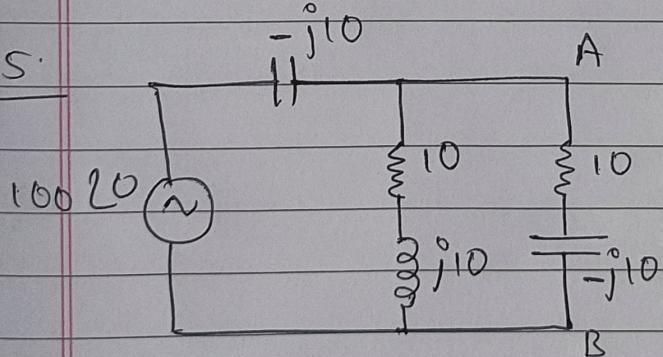

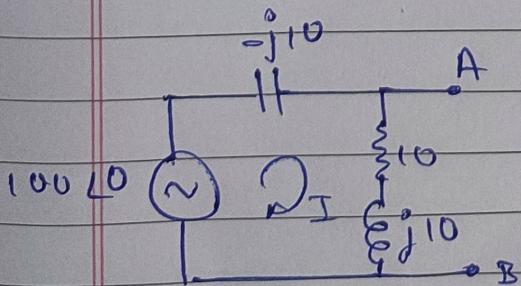Find i flowing AB
using Thevenin's
theorem and
also calculate
power.



$$I = \frac{100 \angle 20^\circ}{10} = 10$$


$$V_{th} = 10(10+j10)$$

$$I_L = 5 \angle 90^\circ$$

$$P = 250 \text{ W}$$


CLASSEMATE

Date _____
Page _____

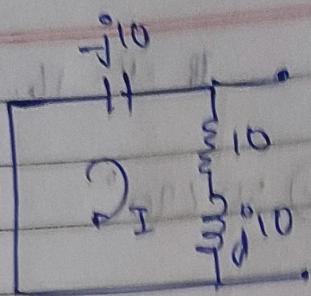

$$Z_m = \frac{(10 + j10)(-j10)}{10 + j10 - j10}$$

$$= -10j + 10$$

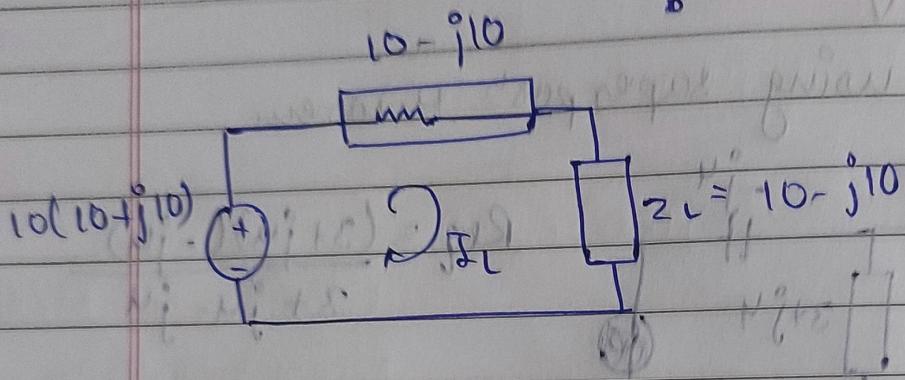

$$I_{LW} = \frac{(10 + j10)}{10 - j10}$$