

Three phase Ac circuits

Introduction


Phase sequence

Connection of 3φ Ac

Power in 3φ Ac

Numericals.

Introduction to 3φ Ac → Polyphase.

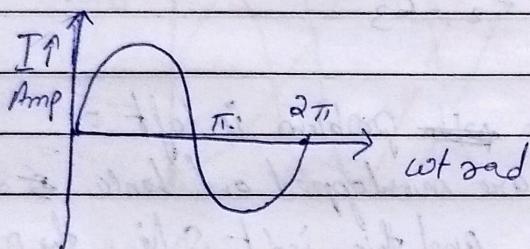


① Device in which we want it to run with an uninterrupted supply = use 3φ Ac.
cos inc in one φ ~~as~~ it approaches zero 3 times in one cycle.

② In that case only from which we are creating 3φ, we can create 3φ, it would be more economical.


why not 2φ, 4φ, 5φ?

Bcoz general device don't need this much of supply.
Phase diff of 180° is provided, so it will start canceling its own phase system.

Generation of three phase Ac

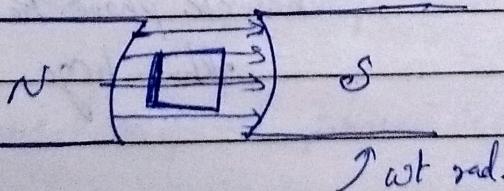

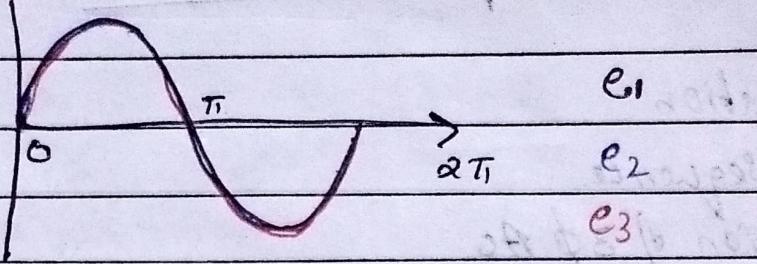Same as 1φ, difference is we have kept 3 conductors on one another.



Condition \rightarrow ① $N_1 = N_2 = N_3$ $e = -Nd\phi/dt$
 $\Rightarrow e_1 = e_2 = e_3$
 ② $\omega_1 = \omega_2 = \omega_3$ ③ $\phi_1 = \phi_2 + \phi_3$
 $\Rightarrow \phi_1 = \phi_2 = \phi_3$

Problem = only one ~~problem~~ problem is left =
 conductors are overlapped and hence, ~~sin~~ wave
 is also overlapped, and this isn't solving the problem
 of approaching zero 3 times.

\Rightarrow For this we have to put 3 of them with some
 ϕ diff., so that if one is at zero, another one isn't.

Phase diff. angle = $\frac{360}{N}$ Electrical degrees

Eg $\phi = \frac{360}{3} \rightarrow$ a cycle has 360°
 $\rightarrow 3\phi$ system

$\phi = 120^\circ$
 \hookrightarrow har ek phase ke bich 120° ka diff.
 rakhna hogा.




$$N_1 = N_2 = N_3$$

$$\omega_1 = \omega_2 = \omega_3$$

$$\phi_1 \neq \phi_2 \neq \phi_3$$

hence $e_1 \neq e_2 + e_3$

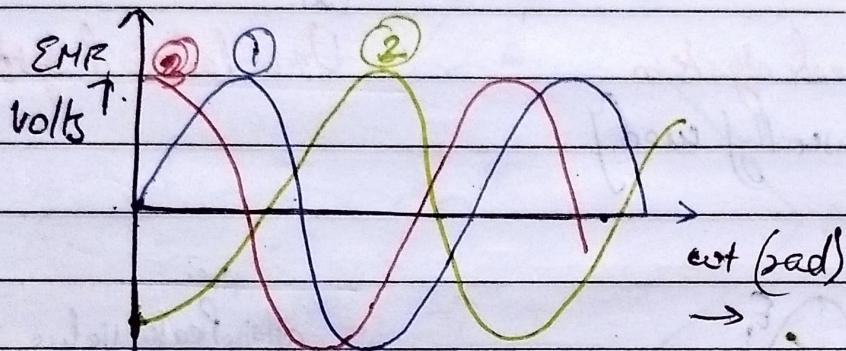magnitude of emf is same
but diff is just ϕ diff.




~~Ans~~ There is not a single time when all 3 will approach zero along with each other.

$$e_1 = E_m \sin \omega t$$

$$e_2 = E_m \sin(\omega t - \frac{2\pi}{3})$$
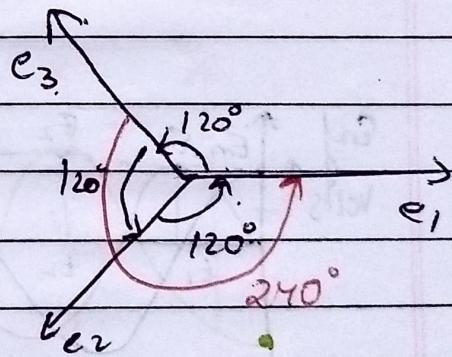
$$e_3 = E_m \sin(\omega t - \frac{4\pi}{3})$$



Phase Sequence:

It is a sequence or order in which the alternating quantities attain their positive peak values.

Universal accepted phase sequence = R Y B
Red \leftarrow Yellow \leftarrow Blue

Types of 3 phase AC

Symmetrical.

(2) Unsymmetrical

i) Source Symmetry

$$N_1 = N_2 = N_3 \text{ or } N_1 + N_2 = N_3$$

ii) Load $\omega_1 = \omega_2 = \omega_3$


Only phase diff. is here

Phase toh hoga hi hoga Sath aur kah bhi.


Balanced system

Unbalanced system.

{Mostly (usually) used}

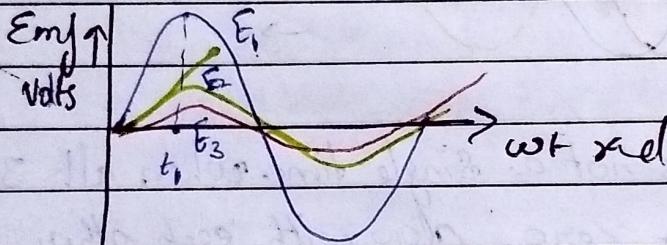

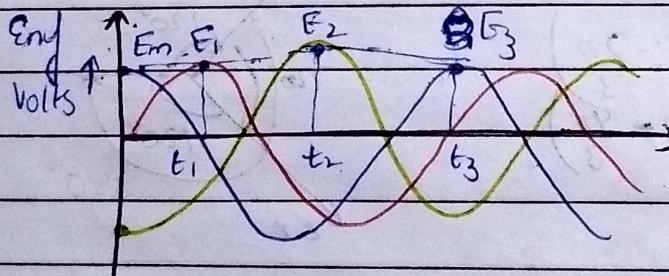attain Peak value = same instant
magnitude = diff



attain Peak value = diff instant
magnitude = same

The quantity which attains its true peak value first (in less time) is said to be leading from others.


E₁ is leading E₂ & E₃ from

E₂ is leading E₃ from

+ive phase sequence = R Y B
-ive " " " = B Y R

Delta connection

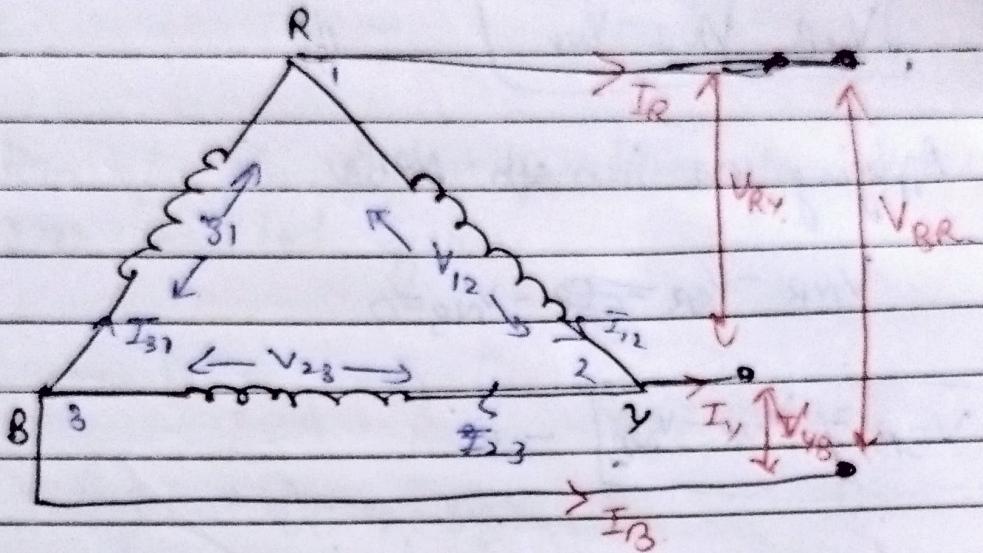It is a type of connection of 3 phase winding where all the coils are connected in a back to back arrangement.



Line quantities :-

$$\text{line voltage} = V_{RY} = V_{BY} = V_{YB} \therefore = V_L$$

$$\text{line current} = I_R = I_Y = I_B = I_L$$

Phase quantities :-

$$\text{Phase voltages } V_{12} = V_{23} = V_{31} = V_{ph}$$

$$\text{Phase current } I_{12} = I_{23} = I_{31} = I_{ph}$$

Relation b/w Line & phase voltage

$$V_{RY} = V_{12}$$

$$V_{23} = I_{YB}$$

$$V_{31} = V_{BY}$$

$$V_{12} = V_{ph}$$

Relation b/w Line & phase current

By KCL at junction R

$$I_{31} - I_{12} - I_R = 0$$

$$\boxed{I_R = I_{31} - I_{12}} \quad \text{--- (1)}$$

By KCL at junction Y

$$I_{12} - I_{23} - I_Y = 0$$

$$\boxed{I_Y = I_{12} - I_{23}}$$

By KCL at junction B

$$I_{23} - I_{31} - I_B = 0$$

$$\boxed{I_B = I_{23} - I_{31}}$$

$$I_R = \sqrt{I_{31}^2 + I_{12}^2 + 2 \times I_{31} I_{12} \cos \phi}$$

$$= \sqrt{I_{ph}^2 + I_{ph}^2 + 2 \times I_{ph}^2 \cos 60^\circ}$$

$$\boxed{I_L = \sqrt{3} I_{ph}}$$

