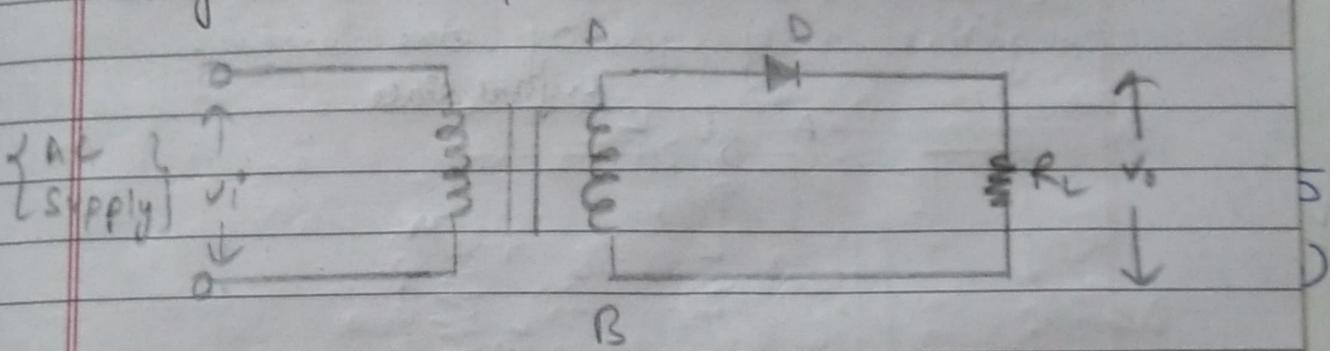


Electronics Assignment - I

Name :- Nikita Singh
 Branch :- Electronics Engineering
 Roll no:- 200106049.

Half wave rectifier.




Characteristics :-

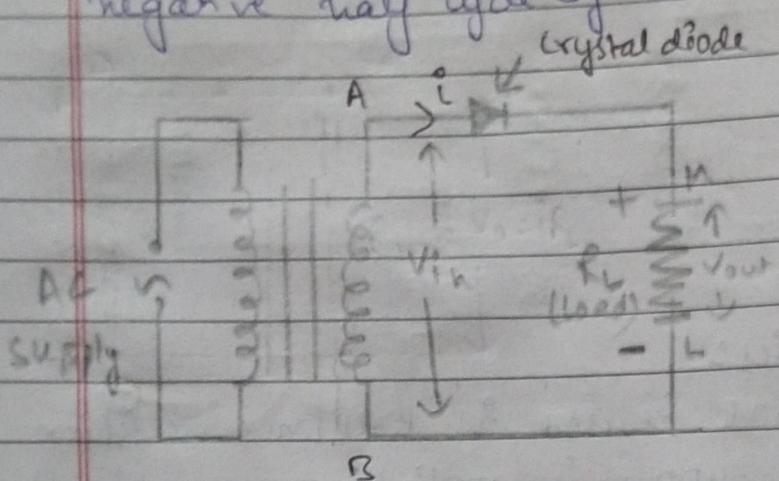
- (i) Single diode is used in half wave rectifier
- (ii) When a.c supply is applied to the input, only positive half cycle appears across the load, whereas, the negative half cycle is suppressed.
- (iii) Step down transformer is used.

Working :- When a.c supply is switched on, the alternating voltage (V_{in}), as shown in fig. (A), appears across the terminal AB at secondary winding. During positive half cycle, the terminal A is positive w.r.t B and the crystal diode is forward biased. Therefore, it conducts current 'i' flows through the load resistor R_L . This current varies in magnitude. Thus, a positive half cycle of output negative $V_{out} = iR_L$ appears across the load resistor (R_L).

During negative half cycles the terminal A is negative w.r.t B and the crystal diode is reverse biased. Under this condition, the diode does not conduct and no current flows through the circuit. Therefore no voltage appears across the load resistor R_L in the negative half cycle of the input.



Waveform

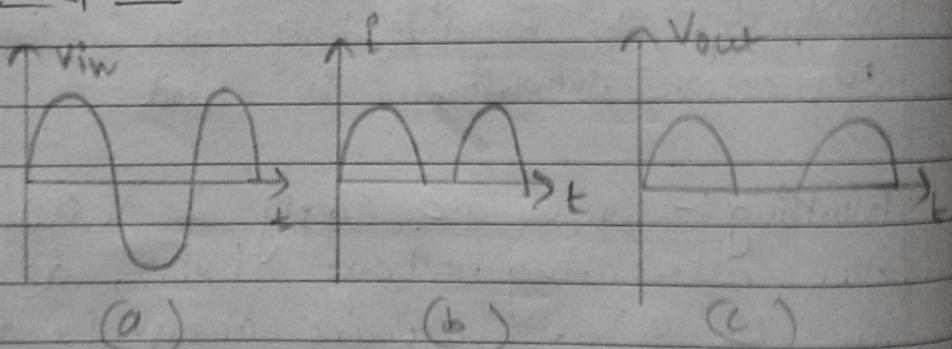

Ripple factor

$$RF = \frac{\text{rms value of ac component of o/p}}{\text{dc value}}$$

$$V_{rms}^2 = V_{(ac)rms}^2 + V_{dc}^2$$

$$\sqrt{V_{(ac)rms}} = \sqrt{V_{rms}^2 - V_{dc}^2}$$

$$RF = \frac{\sqrt{V_{rms} - V_{dc}}}{V_{dc}}$$

$$RF = \frac{V_{dc} \sqrt{\left(\frac{V_{rms}}{V_{dc}}\right)^2 - 1}}{V_{dc}}$$

$$RF = \sqrt{(F.F)^2 - 1} \quad F.F \rightarrow \text{form factor.}$$

$$F.F = \frac{V_{rms}}{V_{avg}} = \frac{V_m/2}{V_m/\pi} = \frac{\pi}{2} = 1.57$$

$$RF = \sqrt{(1.57)^2 - 1}$$

$$[RF = 1.21]$$

Efficiency:-

$$\eta \% = \frac{O/P \text{ DC Power}}{I/P \text{ AC Power}} \times 100 \%$$

$$= \frac{I_{dc}^2 \cdot R}{I_{rms}^2 \cdot R} \times 100 \%$$

$$= \frac{I_m^2 / \pi^2}{I_m^2 / 4} \times 100 \% = \frac{4}{\pi^2} \times 100 \%.$$

$$(I_{dc} = I_m / \pi) \quad [I_{rms} = I_m / 2] \quad [\eta \% = 40.56 \%]$$

% regulation.

$$\% \text{ regulation} = V_{dc}(\text{no load}) - V_{dc}(\text{full load})$$

$$\% \text{ regulation} = \frac{V_{dc}(\text{no load}) - V_{dc}(\text{full load})}{V_{dc}(\text{full load})} \times 100$$

$$V_{dc}(\text{no load}) = V_m / \pi$$

$$V_{dc}(\text{full load}) = I_{dc} \times R_L = \frac{I_m}{\pi} \times R_L$$

$$= \frac{V_m R_L}{\pi (R_L + R_s + R_f)}$$

$$\left. \begin{array}{l} I_m = \frac{V_m}{R_L + R_s + R_f} \end{array} \right\}$$

On putting these values in eqn.

$$\% \text{ regulation} = \frac{\frac{V_m}{\pi} - \frac{V_m R_L}{\pi (R_L + R_s + R_f)}}{\frac{V_m R_L}{\pi (R_L + R_s + R_f)}} \times 100\%$$


$$= \frac{\frac{V_m}{\pi}}{\frac{V_m R_L}{\pi (R_L + R_s + R_f)}} \left(1 - \frac{R_L}{R_L + R_s + R_f} \right) \times 100\%$$

$$\Rightarrow \frac{R_L + R_s + R_f - R_L}{R_L} \times 100\%$$

$$\left. \begin{array}{l} \% \text{ regulation} = \frac{R_s + R_f}{R_L} \times 100\% \end{array} \right\}$$

full wave rectifier :-

- Centre tap rectifier.

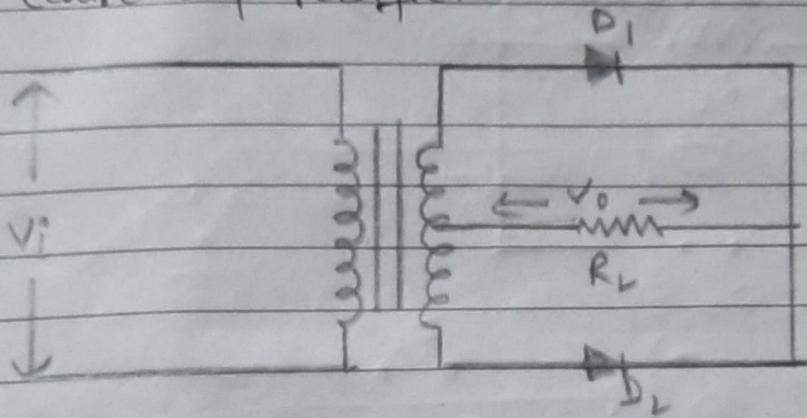

Characteristics:-



→ Two diodes are used in full wave centre tapped rectifier.

→ Secondary winding of transformer is centre tapped for using TUF (Transformer Utilisation factor).


Working:-

During positive half cycle, diode D_1 become forward biased and act as short circuit and diode D_2 become reverse bias and act as open circuit. Diode D_1 conduct the current through R_L and gives O/P.

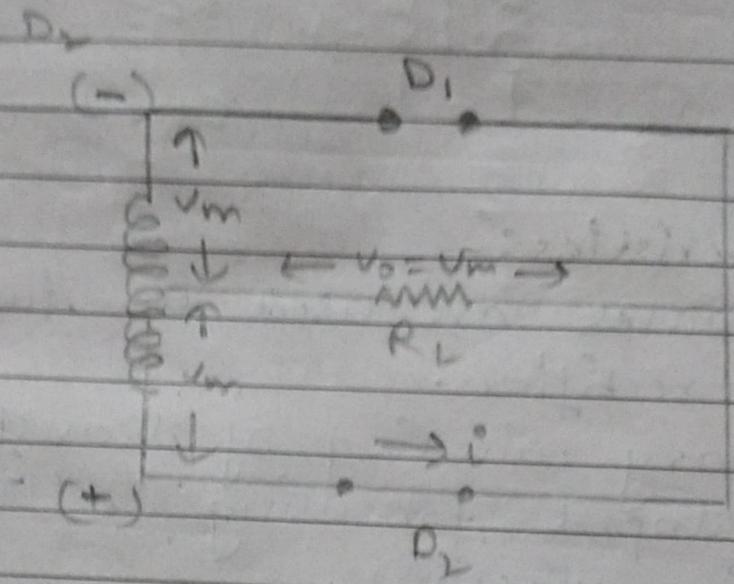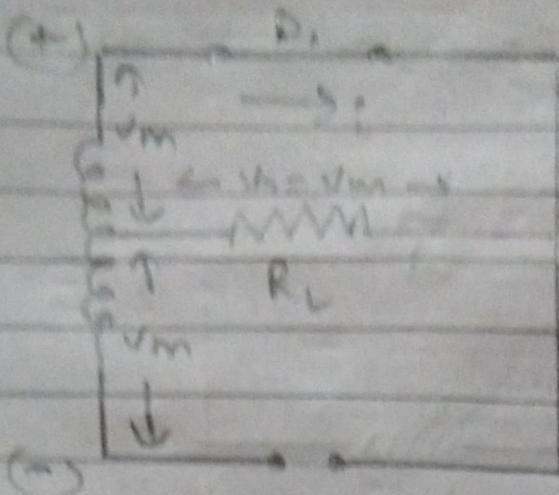
During the negative half cycle, diode D_2 become reverse bias and act as open circuit and diode D_1 become forward bias and act as short circuit diode D_2 conducts the current through load resistance R_L and gives output.



Waveform.

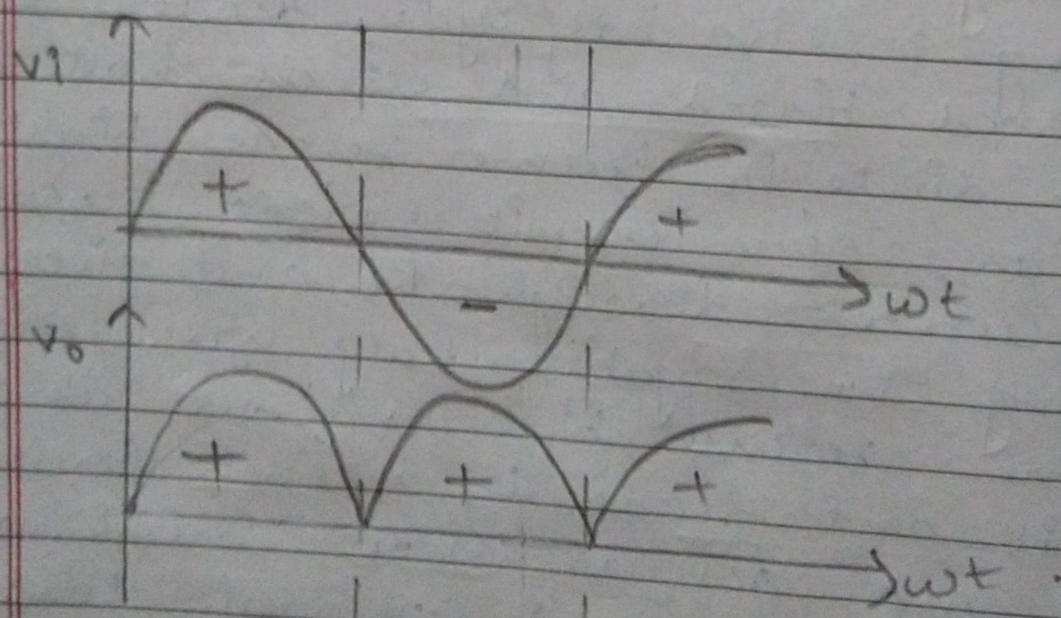

Bridge Rectifier.


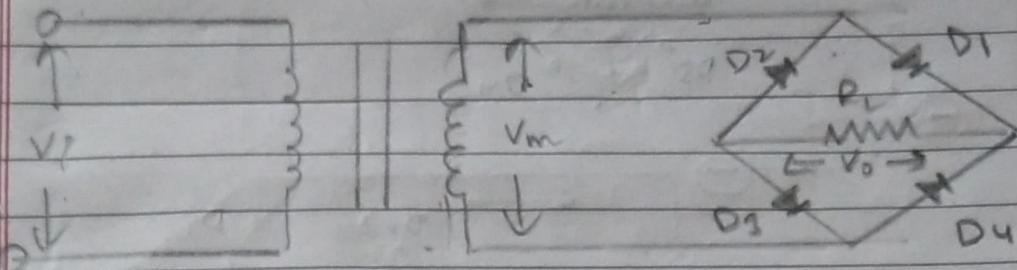


Characteristics.

- 4 diodes are used in bridge rectifier.
- Bridge rectifier offers full wave rectification.
- Bridge combination of diode is connected with secondary winding of transformer.

Working:- During positive half cycle, diode D_1 and D_3 become forward bias and D_2 , D_4 become reverse bias. Diode D_2 and D_4 act as short circuit and passes the current through R_L . Diode D_1 and D_3 act as open circuit and do not conduct the current.

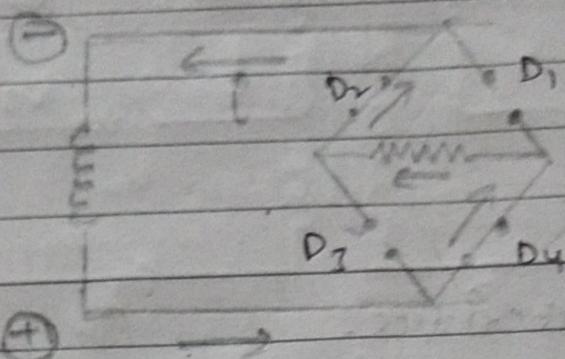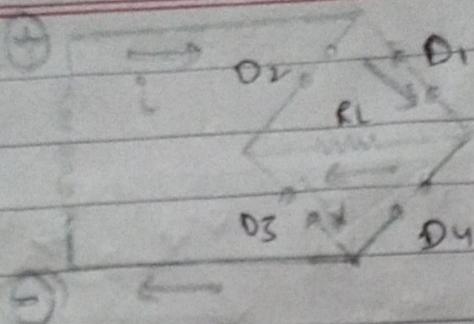During the negative half cycle, D_2 & D_4 act as forward bias and D_1 and D_3 become reverse bias. Diode D_2 and D_4 act as short circuit and D_1 , D_3 act as open circuit. D_2 and D_4 conduct the current through R_L .



Ripple factor

$$RF = \sqrt{(F.F)^2 - 1}$$

$$F.F = \frac{V_{rms}}{V_{avg}} = \frac{V_m/\sqrt{2}}{2V_m/\pi} = \frac{\pi}{2\sqrt{2}} = 1.11$$

$$RF = \sqrt{(1.11)^2 - 1}$$

$$(RF = 0.48)$$

Efficiency

$$\eta \% = \frac{O/P \text{ DC Power}}{I/P \text{ AC Power}} \times 100$$

$$= \frac{I_{dc}^2 R}{I_{rms}^2 R} \times 100 \%$$

$$= 4 \frac{I_m^2 / \pi^2}{I_m^2 / 2} \times 100 \%$$

$$\left\{ \begin{array}{l} I_{dc} = 2I_m / \pi \\ I_{rms} = I_m / \sqrt{2} \end{array} \right.$$

$$= \frac{Q}{\pi^2} \times 100\%$$

$$= [Q\% = 81.13\%]$$

% Regulation

$$\% \text{ regulation} = \frac{V_{dc}(\text{no load}) - V_{dc}(\text{full load})}{V_{dc}(\text{full load})} \times 100\%$$

$$V_{dc}(\text{no load}) = \frac{2V_m}{\pi}$$

$$V_{dc}(\text{full load}) = \frac{2V_m}{\pi} \cdot \frac{R_L}{R_s + R_L + R_f}$$

$$\% \text{ regulation} = \frac{2V_m}{\pi} - \frac{2V_m}{\pi} \left\{ \frac{R_L}{R_s + R_L + R_f} \right\}$$

$$\frac{2V_m}{\pi} \cdot \frac{R_L}{R_s + R_L + R_f}$$

$$= \frac{\frac{2V_m}{\pi} \left\{ 1 - \frac{R_L}{R_s + R_L + R_f} \right\}}{\frac{2V_m}{\pi} \cdot \frac{R_L}{R_L + R_s + R_f}}$$

$$\left[\% \text{ Regulation} = \frac{R_f + R_s}{R_L} \times 100\% \right]$$

→ Comparative Study of half wave, Centre tap and bridge rectifier.

	Half wave	Centre tap	Bridge
Ripple factor	1.21	0.48	0.40
efficiency	40.6%	81.13%	81.13%
% regulation	0%	0%	0%